

PHASOR AND RECTANGULAR CONCEPT :-

- i) $a+bi$ is in Rectangular form
- ii) r/θ is in polar form or Phasor form.

where r is the Radius (ϕ) Magnitude
 θ is the Angle (phase angle difference)

CONVERSION FROM RECTANGLE FORM TO POLAR FORM :-

$$\Rightarrow a+bi \rightarrow r = \sqrt{a^2+b^2} \quad (\text{FIRST QUADRANT})$$
$$\theta = \tan^{-1}(b/a)$$

$$\Rightarrow -a+bi \rightarrow r = \sqrt{a^2+b^2} \quad (\text{SECOND QUADRANT})$$
$$\theta = \pi - \tan^{-1}(b/a)$$

$$\Rightarrow -a-bi \rightarrow r = \sqrt{a^2+b^2} \quad (\text{THIRD QUADRANT})$$
$$\theta = \pi + \tan^{-1}(b/a)$$

$$\Rightarrow a-bi \rightarrow r = \sqrt{a^2+b^2} \quad (\text{FOURTH QUADRANT})$$
$$\theta = -\tan^{-1}(b/a)$$

Eg:- 1. (a) $3+4i \rightarrow r_1/\theta_1$ calculate $r_1, r_2, r_3, r_4, \theta_1, \theta_2, \theta_3$ & θ_4 .

(b) $-3+4i \rightarrow r_2/\theta_2$

(c) $-3-4i \rightarrow r_3/\theta_3$

(d) $3-4i \rightarrow r_4/\theta_4$.

Sol:-

(a) $3+4i \rightarrow \sqrt{3^2+4^2} \angle \tan^{-1}(4/3) = 5 \angle 53.13^\circ$

(b) $-3+4i \rightarrow \sqrt{3^2+4^2} \angle \pi - \tan^{-1}(4/3) = 5 \angle 180 - 53.13^\circ$
 $= 5 \angle 126.86^\circ$

(c) $-3-4i \rightarrow 5 \angle \pi + \tan^{-1}(4/3) = 5 \angle 233.13 = 5 \angle -126.86^\circ$

(d) $3-4i \rightarrow 5 \angle -\tan^{-1}(4/3) = 5 \angle -53.13^\circ$

$r_1 = 5$	$\theta_1 = 53.13^\circ$
$r_2 = 5$	$\theta_2 = 126.86^\circ$
$r_3 = 5$	$\theta_3 = -126.86^\circ$
$r_4 = 5$	$\theta_4 = -53.13^\circ$

CONVERSION FROM POLAR TO RECTANGULAR FORM:-

$$\rightarrow r \angle \theta = r \cos \theta + i(r \sin \theta)$$

Q. Convert $5 \angle 30^\circ$ and $5 \angle -120^\circ$ into Rectangular form.

Sol:-


$$5 \angle 30^\circ = 5 \cos 30^\circ + i(5 \sin 30^\circ) = 4.33 + i(2.5)$$
$$5 \angle -120^\circ = 5 \cos(-120^\circ) + i(5 \sin(-120^\circ)) = -2.5 + i(-4.33)$$
$$= -2.5 - i(4.33)$$

\Rightarrow Graphical Representation of polar form and Rectangular form.


Q. Represent $3+4i$ in polar and Rectangular form.

Sol:-

$$3+4i = 5 \angle 53.13^\circ$$

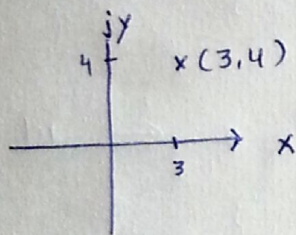

Rectangular form.

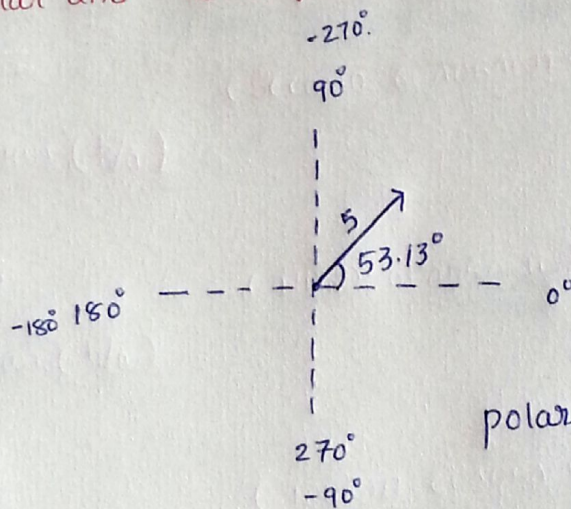

polar (or) phasor Representation

Q. Represent the following in polar form.




- i) $5j$ ii) $-3j$ iii) $1+3j$

Sol:-

$$i) 5j = 0+5j = 5 \angle \tan^{-1}\left(\frac{5}{0}\right) = 5 \angle 90^\circ$$


$$ii) -3j = 0-3j = 3 \angle -90^\circ = 3 \angle -90^\circ$$
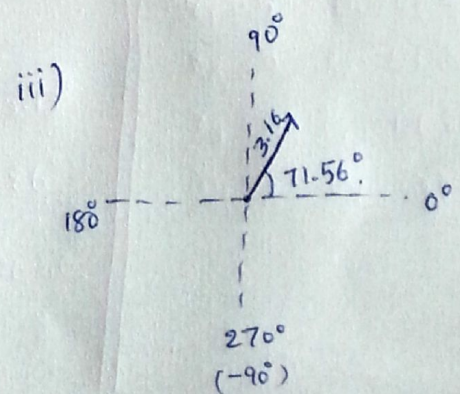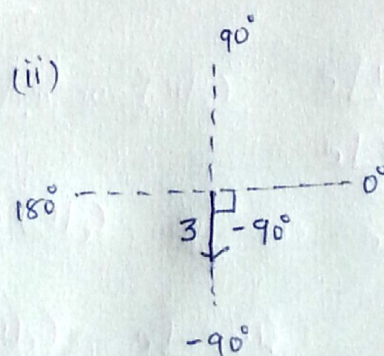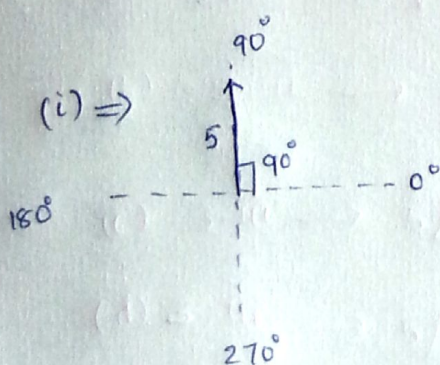
$$iii) 1+3j = \sqrt{1+9} \angle \tan^{-1}(3) = 3.16 \angle 71.56^\circ$$



LEADING, LAGGING AND IN, OUT PHASE CONCEPT IN R, L, C CIRCUITS :-

i) purely Resistive Circuit :-

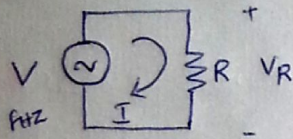


$$-V + IR = 0$$

$$\Rightarrow V = IR$$

$$= IR \angle 0^\circ$$


$$V_R = IR = IR \angle 0^\circ$$

Phasor Representation

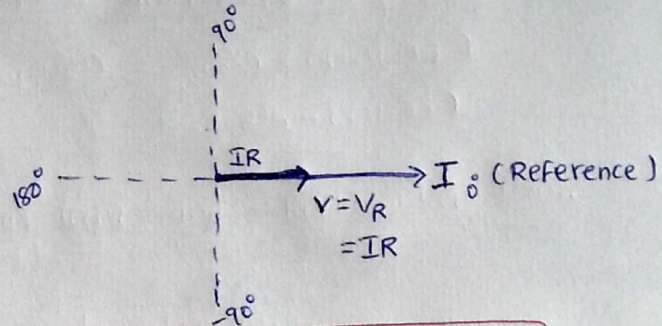

V and I are in same phase

ii) purely Capacitive Circuit :-

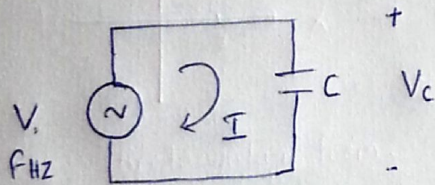


$$-V + jIX_C = 0 \quad ; \quad X_C = \frac{1}{2\pi fC} \Omega$$

$$\Rightarrow V = -IX_C j$$

$$= IX_C \angle -90^\circ$$

$$V_C = IX_C \angle -90^\circ = V$$


Phasor Representation

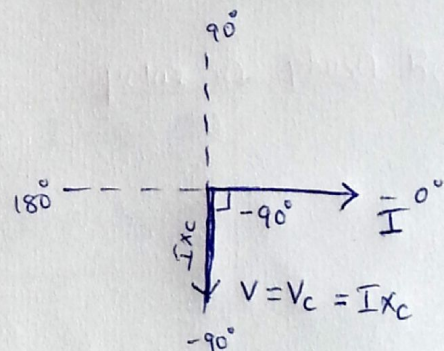

I leads V by 90°
(or)

V lags I by 90°

iii) purely Inductive Circuit :-

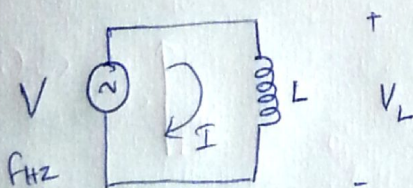


$$X_L = 2\pi fL \Omega$$

$$-V + IjX_L = 0$$

$$\Rightarrow V = IX_L j$$

$$= IX_L \angle 90^\circ = V_L$$

Phasor representation

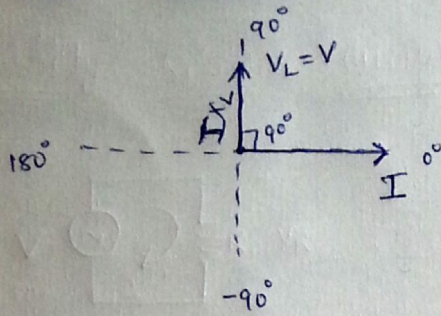


V lead I by 90°

or

I lags V by 90°

SERIES RL Circuit :-

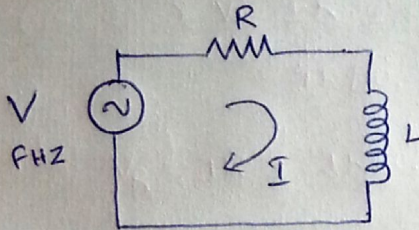

$$-V + IR + j(IX_L) = 0$$

$$X_L = \omega L \Omega$$

$$= 2\pi f L \Omega$$

$$\Rightarrow V = IR + j(IX_L)$$


$$= V_R + jV_L$$

$$|V| = \sqrt{V_R^2 + V_L^2}$$

$$V_R = IR = IR \angle 0^\circ$$

$$V_L = IX_L j = IX_L \angle 90^\circ$$


Phasor Representation :-

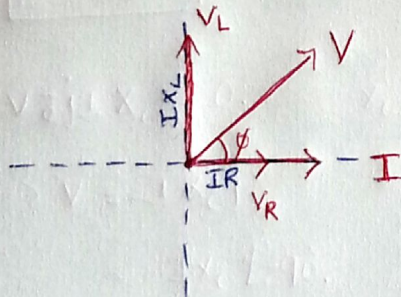

V lead I by ϕ

I lags V by ϕ


SERIES RC CIRCUIT :-

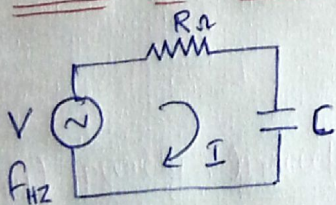

$$X_C = \frac{1}{2\pi f C} \Omega$$

$$V_R = IR = IR \angle 0^\circ$$
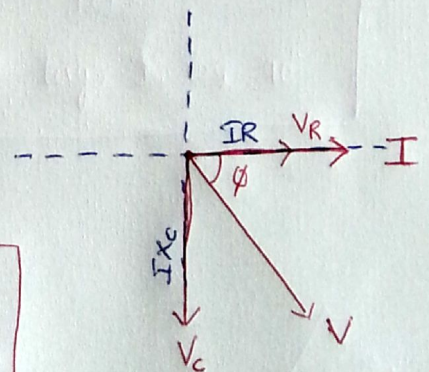
$$V_C = -IX_C j = IX_C \angle -90^\circ$$



I leads V by ϕ

V lags I by ϕ

$$-V + IR - jIX_C = 0$$

$$\Rightarrow V = IR - jIX_C$$

$$= V_R - jV_C$$

$$|V| = \sqrt{V_R^2 + V_C^2}$$

Resonance concept (Not in syllabus)

→ The Frequency at which Inductive Reactance is equal to Capacitive Reactance is known as Resonance Frequency

$$X_L = X_C$$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow 2\pi f L = \frac{1}{2\pi f C}$$

$$\Rightarrow (2\pi f)^2 = \frac{1}{LC}$$

$$\Rightarrow \boxed{f = \frac{1}{2\pi\sqrt{LC}}}$$

NUMERICAL (Eg:)

Q How much voltage is necessary to flow a current of 20 milli Ampere through the Series RC Circuit having Resistance of 100Ω and Capacitance of $50\mu\text{Farad}$ at 100Hz .

Sol:- Given data, $I = 20$ milli Ampere

$$R = 100\Omega$$

$$V = ?$$

$$C = 50\mu\text{F}$$

$$f = 100\text{Hz}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi(100)(50) \times 10^{-6}} = 31.83\Omega$$

By Applying KVL,

$$-V + 100I - j(31.83)I = 0$$

$$\Rightarrow V = I(100 - j31.83)$$

$$= 20 \times 10^{-3} (100 - j31.83)$$

$$|V| = 20 \times 10^{-3} \sqrt{100^2 + 31.83^2}$$

$$= \underline{\underline{2.09 \text{ Volt}}}$$

∴ 2.09 Volts is necessary.

