


AC - CIRCUITS

①

→ * Alternating Current or Voltage wave form :-

- * Alternating Current or Voltage is one the Circuit direction to which reverses at regularly recurring intervals.
- * one Complete set of positive and negative values of alternating quantity is known as cycle.

Eg:-

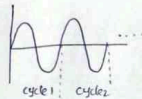


This wave form completes two cycles

- * The time taken by an alternating quantity to complete one cycle is called its time period (T). units of time is seconds.

- * The no. of cycles/second is called Frequency of alternating quantity. units of Frequency is Hertz. (or) $\text{Frequency} = f = \frac{1}{\text{Time period}} = \frac{1}{T}$

- * Maximum value (either positive or negative) of an AC quantity (Alternating) is known as its Amplitude

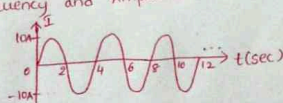⑤. Calculate T, Frequency and Amplitude for the following wave form.



Sol:- Time period = T = 4 sec.

$$\text{Frequency} = f = \frac{1}{T} = \frac{1}{4} \text{ Hz} = 0.25 \text{ Hz}$$

$$\text{Amplitude} = 10 \text{ V}$$

- * Phase :- The fraction of the time period of the Alternating Current which has elapsed since the current last passed through zero position of reference.

Scanned by CamScanner

→ There are Several methods to express Amplitude value. ②
Eg. peak Amplitude value, peak-peak value, RMS value, Avg value... etc.* Mathematical Representation and Definitions of AC wave form :-

→ Alternating Current wave form represented mathematically as follows.

$$i(t) = I_p \sin(\omega t + \phi)$$

where I_p = peak value of wave form. (Amplitude) (Amps)


$$\omega = 2\pi f = \frac{2\pi}{T} = \text{Angular Frequency (rad/sec)}$$

 f = Frequency of the wave form. (Hertz)

$$T = \frac{1}{f} = \text{Time period of the waveform (sec)}$$

 ϕ = phase differenceIf $\phi = 0$ means, $i(t)$ is having phase of 0° and phase difference 0.

⑥. Express the following sine wave form in Mathematical form.

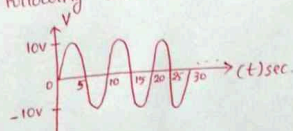Sol:- peak value or Amplitude = $V_p = 10 \text{ V}$.

$$\text{Time period} = T = 10 \text{ sec.}$$

$$\text{Frequency} = f = \frac{1}{T} = \frac{1}{10} = 0.1 \text{ Hz}$$

$$\text{Angular Frequency} = \omega = 2\pi(f) = 2\pi(0.1) = 0.2\pi \text{ rad/sec.}$$

Phase = $\phi = 0$ (Because the wave form started at zero only)

$$V(t) = V_p \sin(\omega t + \phi)$$

$$V(t) = 10 \sin(0.2\pi t)$$

Scanned by CamScanner

→ Root Mean Square Value Calculation for an AC signal:

* The RMS value of an AC current is given by the steady current (DC current) which when flowing through a given circuit for a given time produces the same heat as produced by alternating current when flowing through the same circuit for the same time.

* RMS Value is also known as Effective Value.

* Mathematically, RMS value for any periodic signal is given by.

$$I_{rms} = \text{RMS value} = \sqrt{\frac{1}{T} \int_0^T I^2(t) dt}$$

* For an AC signal (sinusoidal signal) $I(t) = I_m \sin(\omega t)$, I_{rms} is given by

$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{T} \int_0^T (I_m \sin(\omega t))^2 dt} \\ &= \left[\frac{1}{T} \int_0^T I_m^2 \sin^2(\omega t) dt \right]^{1/2} \\ &= \left[\frac{1}{T} \int_0^T I_m^2 \frac{1 - \cos(2\omega t)}{2} dt \right]^{1/2} \\ &= \left(\frac{1}{T} \int_0^T \frac{I_m^2}{2} dt \right)^{1/2} = \left(\frac{1}{T} \cdot \frac{I_m^2}{2} \cdot T \right)^{1/2} = \frac{I_m}{\sqrt{2}} \end{aligned}$$

$$\therefore I_{rms} = \frac{I_m}{\sqrt{2}}$$

→ Average Value Calculation for a Sinusoidal Signal:-

* Average value I_{avg} of an AC is expressed by the steady (DC) current which transfers across any circuit the same charge as is transferred by that alternating current during the same time.

$$I_{avg} = \frac{1}{T} \int_0^T I(t) dt$$

* For an AC signal $I(t) = I_m \sin \omega t$, I_{avg} is given by

$$\begin{aligned} I_{avg} &= \frac{1}{T} \int_0^T I_m \sin \omega t dt \\ &= \frac{1}{T} \left[-\frac{I_m \cos \omega t}{\omega} \right]_0^T = -\frac{I_m}{T} \left[\frac{\cos(2\pi/T) - \cos(0)}{2\pi/T} \right] \\ &= -\frac{I_m}{T} \cdot \frac{T}{2\pi} [-1 - 1] = \frac{I_m}{\pi} = 0.637 I_m \end{aligned}$$

$$I_{avg} = \frac{I_m}{\pi}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

For sinusoidal wave form:

* Form Factor = $K_f = \frac{\text{rms value}}{\text{Avg. Value}} = \frac{I_m/\sqrt{2}}{I_m/\pi} = 1.11$

* Crest or peak or Amplitude factor = $\frac{\text{Maximum value}}{\text{rms value}} = \frac{\text{Peak value}}{\text{rms value}} = \frac{I_m}{I_m/\sqrt{2}} = \sqrt{2}$

→ Rectangle to polar form conversion (will be discussed in class)

→ Addition and subtraction of AC wave forms (in polar form)

* In polar form, i) $V(t) = V_m \sin(\omega t + \phi)$ will be represented as $V_m \angle \phi$
ii) $V(t) = V_m \cos(\omega t + \phi)$ will be represented as $V_m \angle 90 + \phi$

(I have written formulas taking Sine wave as reference).

⑨. Add $200 \sin \omega t + 100 \sin(\omega t + 30^\circ) = 290.93 \angle 9.89^\circ$

Sol:- $200 \angle 0^\circ + 100 \angle 30^\circ = 290.93 \angle 9.89^\circ$

⑩. $10 \sin(\omega t + 30^\circ) + 20 \cos(\omega t + 45^\circ) + 10 \cos(\omega t - 10^\circ) = 33.33 \angle 102.61^\circ$


Sol:- $10 \angle 30^\circ + 20 \angle (90+45) + 10 \angle (90-10) = 33.33 \angle 102.61^\circ$

→ RMS value and Average Value Calculation for Non-Sinusoidal waveform

$$V_{rms} = \left[\frac{1}{T} \int_0^T V^2(t) \cdot dt \right]^{1/2}$$

$$V_{avg} = \frac{1}{T} \int_0^T V(t) \cdot dt$$

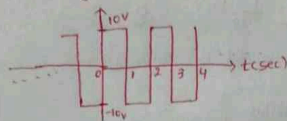Q. what is the average value and RMS value for the following waveform.



Sol:- $V(t) = 10 \quad (0 \leq t \leq 1)$
 $= -10 \quad (1 < t < 2)$ Time period = 2 sec.

$$\begin{aligned} \therefore V_{avg} &= \frac{1}{T} \int_0^T V(t) \cdot dt = \frac{1}{2} \int_0^2 V(t) \cdot dt \\ &= \frac{1}{2} \left[\int_0^1 10 \cdot dt + \int_1^2 (-10) \cdot dt \right] \\ &= \frac{1}{2} \left[10[t]_0^1 + [-10(t)]_1^2 \right] = \frac{1}{2} [10 - 10] = 0 \end{aligned}$$

$$\Rightarrow V_{avg} = 0$$

$$\begin{aligned} V_{rms} &= \left[\frac{1}{T} \int_0^T V^2(t) \cdot dt \right]^{1/2} = \left[\frac{1}{2} \int_0^2 V^2(t) \cdot dt \right]^{1/2} \\ &= \left[\frac{1}{2} \left[\int_0^1 10^2 \cdot dt + \int_1^2 (-10)^2 \cdot dt \right] \right]^{1/2} = \left[\frac{1}{2} [100 + 100] \right]^{1/2} \end{aligned}$$

$$\Rightarrow V_{rms} = 10V$$

$$V_{avg} = 0 \quad V_{rms} = 10V$$

→ Apply Same method for any other non sinusoidal waveform.

→ while dealing with DC circuits, we have done problems with only Resistive element (R). But in AC, we have to consider Reactive elements (L and C) also.

→ Impedance = Resistance + j(Reactance)

→ Imaginary part of impedance is Reactance denoted with X Ω.

→ Real part of Impedance is Resistance denoted with R Ω.

→ In DC circuits, we have only power. But in AC, we have three types of powers.

→ In DC circuits, power will be dissipated across only R.

→ In AC circuits, power will be available across R, L, C also.

→ The power associated with Resistive elements in AC circuit is Real or true power, (denoted by P), units are watt.

→ The power associated with Reactive elements (L and C) combined in AC circuit is Reactive power, (denoted by Q), units are VAR (volt ampere Reactive).

→ The power associated with Impedance in AC circuit is Apparent power, denoted by S, and units are VA, (volt ampere).

→ In AC circuits,
 $R \rightarrow R \Omega$
 $L \rightarrow j\omega L \Omega$ (Equivalent representation)
 $C \rightarrow \frac{1}{j\omega C} \Omega$

→ Reactance across Inductance = $X_L = \omega L \Omega$ (or) $j\omega L$

→ Reactance across Capacitance = $X_C = \frac{1}{\omega C} \Omega$ (or) $\frac{1}{j\omega C}$

Note:- In solving numericals, we will consider j also.



$$j \times j = -1, \quad -\frac{1}{j} = j$$

* DC signal is having frequency Zero. i.e. $f=0 \Rightarrow \omega = 2\pi f = 0$.


→ Concept to solve AC Numericals

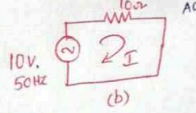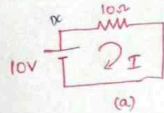i) Resistance (R) :-


Q. Calculate current I in the following Circuits (a) and (b)



sol:-

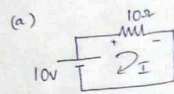

$$-10 + 10I = 0 \\ \Rightarrow I = 1A$$


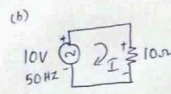


$$-10 + 10I = 0 \\ \Rightarrow I = 1A$$

For AC Circuits
don't take polarity
signs
only for convenience
I have taken.

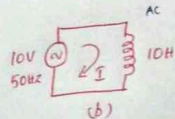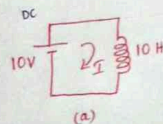ii) Inductance :-

Q. Calculate Current I in the following Circuits (a) and (b).




sol:- For Inductance, convert Inductance into Reactance in both circuits.

(a) For DC, $F = 0 \Rightarrow \omega = 0, L = 10H$

$$X_L = \text{Reactance} = \omega L \Omega \\ = 0(10) \\ = 0 \Omega$$

(a) will be converted as follows.

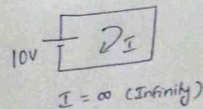

$$I = \infty \text{ (Infinity)}$$


(b) $F = 50\text{Hz}$ (given)

$$L = 10H$$

$$\omega = 2\pi(f) = 2\pi(50) = 100\pi$$

$$X_L = \text{Reactance} = \omega L = 1000\pi \Omega$$

(b) is converted as follows.


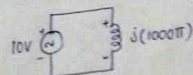


$$I = \frac{10}{j(1000\pi)} = 3.18 \times 10^{-3} \angle -90^\circ$$

$$\therefore I_{\text{rms}} = 3.18 \text{ mA}$$

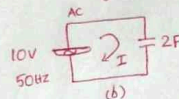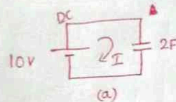iii) Capacitance :-


Q. Calculate current I in the following Circuits (a) and (b).



sol:- (*) $X_C = \frac{1}{j(\omega C)} = \frac{1}{j(2\pi(50)(2))}$

$$= \infty \Omega$$


(a) will be drawn as follows.

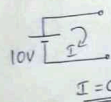

$$I = 0A$$

(b) $X_C = \frac{1}{j(\omega C)} = \frac{1}{j(2\pi(50)(2))} = 1.59 \times 10^{-3} \angle -90^\circ$

(b) will be drawn as follows.

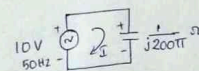

$$I = \frac{10}{j200\pi} = 10(200\pi) \\ = 6283.18 A$$


* Power Concept related Formulas for AC Circuits.

→ power factor :- $\frac{R}{Z}$ in AC circuit. (a) $\cos(\phi)$ where ϕ is the phase difference b/w V and I in circuit (b) $\frac{\text{True power}}{\text{Apparent power}}$ in AC circuit.

→ True power :- $P = V_{\text{rms}} I_{\text{rms}} \cos \phi$ Watt


→ Reactive power :- $Q = V_{\text{rms}} I_{\text{rms}} \sin \phi$ VAR

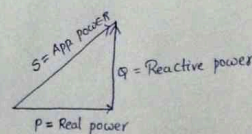→ Apparent power :- $S = V_{\text{rms}} I_{\text{rms}}$ VA $= \sqrt{P^2 + Q^2}$ VA



Power Triangle

→ Series R, L, C Circuit :-

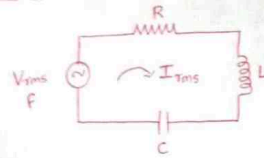

$V_R = \text{---}$	$X = \text{---}$	$P_c = \text{---}$
$V_L = \text{---}$	$I_{rms} = \text{---}$	$P = \text{---}$
$V_C = \text{---}$	$Z = \text{---}$	$Q = \text{---}$
$X_L = \text{---}$	$P_R = \text{---}$	$S = \text{---}$
$X_C = \text{---}$	$P_L = \text{---}$	Power factor = ---


Sol:- Reactance across L = $X_L = \omega L = 2\pi f L \Omega$

Reactance across C = $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \Omega$

Resistance in the circuit = $R \Omega$

Reactance in the circuit = $X = X_L - X_C \Omega$ (or) $X_C - X_L \Omega$

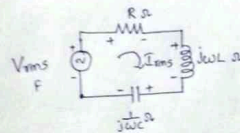The given circuit can be drawn like this.



$$\begin{aligned} \text{Impedance } Z &= R + jX \\ &= R + j(\omega L - \frac{1}{\omega C}) \\ &= \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} \end{aligned}$$

By KVL, $-V_{rms} + I_{rms} \cdot R + j\omega L \cdot I_{rms} + \frac{1}{j\omega C} \cdot I_{rms} = 0$

$$\Rightarrow I_{rms} = \frac{V_{rms}}{R + j(\omega L - \frac{1}{\omega C})} = \frac{V_{rms}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{V_{rms}}{Z}$$

→ power factor = $\frac{R}{Z} = \cos \phi \Rightarrow \phi = \cos^{-1}(R/Z)$

→ $V_R = I_{rms} \cdot R \Rightarrow P_R = P = \text{power across Resistor} = I_{rms}^2 \cdot R = V_{rms} I_{rms} \cos \phi$

→ $V_L = I_{rms} \cdot \omega L \Rightarrow P_L = V_L \cdot I_{rms} = I_{rms}^2 \cdot \omega L$



→ $V_C = I_{rms} \cdot \frac{1}{\omega C} \Rightarrow P_C = V_C \cdot I_{rms} = I_{rms}^2 \cdot \frac{1}{\omega C}$

→ $P_L - P_C = Q = \text{Reactive power} = V_{rms} I_{rms} \sin \phi$

→ $S = V_{rms} I_{rms} = \text{Apparent power}$

Scanned by CamScanner

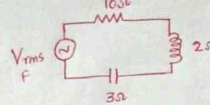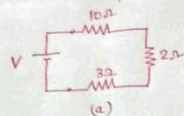⑨ Calculate Impedance for the following circuits (a) and (b)



Sol:- (a) $Z = 10 + 2 + 3$
 $= 15 \Omega$

(b) $Z = R + jX_L - jX_C$
given data is $R = 10 \Omega$ $X_L = 2 \Omega$ $X_C = 3 \Omega$
 $\therefore Z = 10 + j(2 - 3)$
 $= 10 - j \Rightarrow |Z| = \sqrt{10^2 + 1} = 10.04 \Omega$

→ Before this question (above) i.e. 9th qy. we discussed about Series RLC.

Circuit. In that circuit, IF

→ $L = 0, R = 0 \Rightarrow C$ circuit ($C \neq 0$)

→ $C = 0, R = 0 \Rightarrow L$ circuit ($L \neq 0$)

→ $L = 0, C = 0 \Rightarrow R$ circuit ($R \neq 0$)


IF $C = 0 \Rightarrow RL$ circuit (series) ($R \neq 0, L \neq 0$)

$L = 0 \Rightarrow$ Series RC circuit. ($R \neq 0, C \neq 0$)

IF $R \neq 0, L \neq 0, C \neq 0$ then that circuit is Series RLC circuit.

then All the formulas and diagrams will be changed by placing (or) substituting R, L, C values.

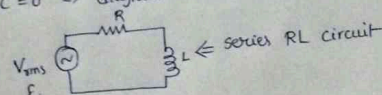
Eg. IF $C = 0 \Rightarrow$ diagram will be written as



IF $R = 0, L = 0 \Rightarrow$ \Leftarrow Capacitor circuit.

Scanned by CamScanner

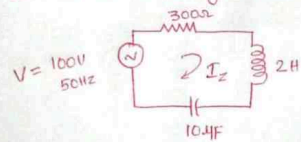⑩. What are the values of $X_L, X_C, X, Z, I_Z, V_L, V_C, V_R, P_R, P_L, P_C$, power factor, P, Q, S for the following circuit.



$$V = V_{rms} = V$$

$$I_Z = I_{rms} = I$$

Sol:- Given data is: $V = V_{rms} = 100V$; $R = 300\Omega$; $L = 2H$; $C = 10.4\mu F$; $f = 50Hz$

$$X_L = \omega L = 2\pi f L = 2\pi(50)(2) = 200\pi \Omega = 628.318\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi(50) \times 10 \times 10^{-6}} = 318.3098\Omega$$

$$X = X_L - X_C = 310.0087\Omega$$


$$Z = |R + j(X_L - X_C)| = \sqrt{R^2 + (X_L - X_C)^2} = 431.359\Omega$$

$$I = I_Z = \frac{V}{Z} = \frac{100}{431.359} = 0.2318A$$

$$V_R = I \cdot R = 0.2318(300) = 69.54V$$

$$V_L = I X_L = 0.2318(628.318) = 145.644V$$
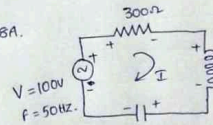
$$V_C = I X_C = 0.2318(318.3098) = 73.784V$$



Verification By KVL, $V + V_R + jV_L - jV_C = 0$
 $\Rightarrow V = \sqrt{V_R^2 + (V_L - V_C)^2}$

$$P = P_R = V_R I = 69.54(0.2318) = 16.113W$$

$$P_L = V_L I = 33.760VAR \quad \left. \begin{array}{l} P_L = P_C = 16.6569VAR \\ P_C = V_C I = 17.1031VAR \end{array} \right\} Q = P_L - P_C = 16.6569VAR$$

$$S = V \cdot I = \text{Apparent power} = 100(0.2318) = 23.18VA$$

You can calculate P, Q, S in another Method by using Direct formulas also. They are $P = VI \cos \phi$, $Q = VI \sin \phi$, $S = \sqrt{P^2 + Q^2}$

Scanned by CamScanner

→ Admittance:-

Admittance of a circuit is defined as the reciprocal of its Impedance. It is denoted with Y . Its unit is Siemens (S).

$$Y = \frac{1}{Z} = \frac{1}{R + jX} = \left(\frac{R}{R^2 + X^2} \right) + j \left(\frac{-X}{R^2 + X^2} \right)$$


$$= G + jB$$

where G = conductance and B = susceptance.

- when $X=0$, conductance G is the reciprocal of Resistance (R)
- when $R=0$, susceptance B is the reciprocal of Reactance (X)
- Admittance (Y) is the Reciprocal of Impedance (Z)

→ In parallel branches Admittances are Added.

* parallel RLC Circuit:-

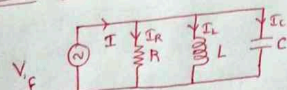

$$V = V_{rms}$$

$$I = I_{rms}$$

$$\rightarrow V_R = V_L = V_C = V$$

$$\rightarrow I_R = \frac{V}{R}$$

$$\rightarrow I_L = \frac{V}{X_L}$$

$$\rightarrow I_C = \frac{V}{X_C}$$

$$\rightarrow I = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$Y = \frac{1}{R} + \frac{1}{jX_L} + \frac{1}{jX_C}$$

$$= \frac{1}{R} + j \left(\frac{1}{X_C} - \frac{1}{X_L} \right)$$

$$= G + jB$$


$$Z = \frac{1}{G + jB}$$

$$P_R = P = VI \cos \phi = I_R^2 R = V I_R$$

$$P_L = V_L I_L \quad \left. \begin{array}{l} P_L = P_C = V I \sin \phi \\ P_C = V_C I_C \end{array} \right\}$$

$$S = VI = \sqrt{P^2 + Q^2}$$

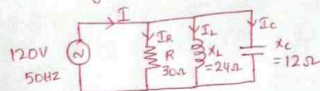Q. What are the values of I , I_R , I_L , I_C , V , P_R , P_L , P_C , P , Q , and S in the following circuit. (13)



Sol:- Given data is $V=120V$, $f=50Hz$, $R=30\Omega$, $X_L=24\Omega$, $X_C=12\Omega$.

$$I_R = \frac{V}{R} = \frac{120}{30} = 4A$$

$$I_L = \frac{V}{X_L} = \frac{120}{24} = 5A$$

$$I_C = \frac{V}{X_C} = \frac{120}{12} = 10A$$

$$I = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$= \sqrt{4^2 + (5 - 10)^2} = \sqrt{41} A$$

$$\Rightarrow I = \sqrt{41} = 6.4031 A$$

$$\Rightarrow P_R = V I_R = 120(4) = 480 W$$

$$P_L = V I_L = 120(5) = 600 VAR$$

$$P_C = V I_C = 120(10) = 1200 VAR$$

$$Q = P_L - P_C = -600 VAR$$

$$= 600 VAR \text{ (Capacitive)}$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{480^2 + 600^2}$$

$$S = 768.37 VA$$

You can calculate and verify your P , Q , S using other formulas also.
i.e. $P = VI \cos \phi$, $Q = VI \sin \phi$, $S = VI$.

* Resonant Frequency :-

In a Series RLC circuit (or) parallel RLC circuit, the frequency at which $X_L = X_C$ is known as resonant frequency (or)

The frequency at which inductive reactance equal to capacitive reactance is known as Resonant frequency.

$$X_L = X_C$$


$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega^2 = \frac{1}{LC}$$


$$\Rightarrow (2\pi f)^2 = \frac{1}{LC} \Rightarrow f_r = \frac{1}{2\pi\sqrt{LC}} \text{ Hertz}$$

Scanned by CamScanner

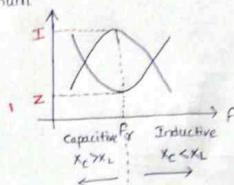→ At Resonance, For Series RLC circuit, Impedance is minimum. So Current is Maximum. power factor is 1 (unity) and circuit is purely resistive.



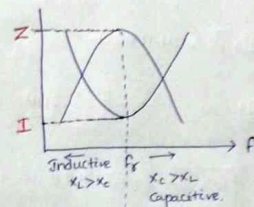→ At Resonance, For parallel RLC circuit, Admittance is minimum. Means Impedance is Maximum and Current is Minimum. power factor is unity (1) and circuit is purely resistive.



→ phasor concepts regarding Series R, L, C, RL, RC, and parallel will be discussed in class.

→ Rectangle to polar and polar to Rectangular conversion will also be explained in class.

⑧. In a series RL circuit,

$$i(t) = 5 \sin(314t + 120^\circ)$$

$$v(t) = 15 \sin(314t + 150^\circ)$$

- Calculate RMS value of current and voltages.
- Average power?
- Real power?
- Reactive power?
- Apparent power?

Sol:- Given data is $i(t) = 5 \sin(314t + 120^\circ)$
 $v(t) = 15 \sin(314t + 150^\circ)$

$$I_{rms} = \frac{5}{\sqrt{2}} ;$$

$$V_{rms} = \frac{15}{\sqrt{2}}$$

$$\phi = 150^\circ - 120^\circ = 30^\circ ; \text{ power factor} = \cos \phi = \cos 30^\circ = 0.866 \text{ (lag)}.$$

$$\cos \sin \phi = \sin 30^\circ = 0.5 ;$$

$$\therefore \text{Average power} = \text{Real power} = I_{rms}^2 R \cos \phi = V_{rms} I_{rms} \cos \phi$$

$$= \frac{5}{\sqrt{2}} \cdot \frac{15}{\sqrt{2}} \cdot \cos 30^\circ = \boxed{32.475 \text{ W}}$$

$$\text{Reactive power} = V_{rms} I_{rms} \sin \phi$$

$$= \frac{5}{\sqrt{2}} \cdot \frac{15}{\sqrt{2}} \cdot \sin 30^\circ = \boxed{18.75 \text{ VAR}}$$

$$\text{Apparent power} = \sqrt{\text{Real power}^2 + \text{Reac power}^2} \quad (\text{or}) \quad V_{rms} I_{rms}$$

$$= \sqrt{32.475^2 + 18.75^2} \quad (\text{or}) \quad \frac{15}{\sqrt{2}} \cdot \frac{5}{\sqrt{2}}$$

$$= \boxed{37.499 \text{ VA}} \quad (\text{or}) \quad 37.5 \text{ VA}$$

Scanned by CamScanner

⑨. In a series RL circuit, the current and voltage expressed as

$$i(t) = 5 \sin(314t + \frac{2\pi}{3}) \text{ and}$$


$$v(t) = 15 \sin(314t + 5\pi/6)$$

- what is the magnitude of Impedance of the circuit?
- Value of Resistance (R)?
- Value of Inductance (L)?
- Average power drawn by the circuit?
- What is the power factor? is it lagging or leading.

Sol:- Given data, $i(t) = 5 \sin(314t + 120^\circ)$
 $v(t) = 15 \sin(314t + 150^\circ)$

$$\text{i.e } \omega = 314 \text{ rad/sec.}$$

$$a) Z = \left| \frac{V(t)}{I(t)} \right| = \frac{15}{5} = 3 \Omega$$

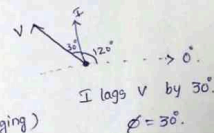

$$e) \text{ power factor} = \cos \phi = \cos 30^\circ = \frac{\sqrt{3}}{2} \text{ (lagging)}$$

$$\Rightarrow \cos \phi = 0.866 \text{ (lag)}$$

$$b) \text{ power factor} = \cos \phi = \frac{R}{Z}$$

$$\Rightarrow 0.866 = \frac{R}{3} \Rightarrow R = 0.866 \times 3 = \boxed{2.59 \Omega}$$

$$c) Z = \sqrt{R^2 + X_L^2} \Rightarrow 3^2 = \sqrt{(2.59)^2 + X_L^2}$$

$$\Rightarrow X_L = \sqrt{9 - 6.75} = 1.5 \Omega$$

$$\text{But } X_L = \omega L \Rightarrow 1.5 = 314(L) \Rightarrow L = \frac{1.5}{314} = \boxed{4.7 \text{ mH}}$$

$$d) \text{ Average power} = V_{rms} I_{rms} \cos \phi$$


$$= \frac{15}{\sqrt{2}} \cdot \frac{5}{\sqrt{2}} \cdot (0.866) \quad \text{or} \quad I_{rms}^2 R$$

$$= 32.5 \text{ W (Approx)}$$

$$= \left(\frac{5}{\sqrt{2}}\right)^2 \cdot 2.59 = \boxed{32.5 \text{ W (Approx)}}$$

Scanned by CamScanner

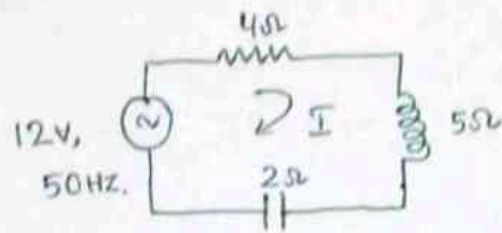Q. In following Series RLC circuit, calculate.



- i) X_L ii) X_C iii) X iv) $|Z|$ v) $|Y|$ vi) V_L vii) V_C .
 viii) V_R ix) I x) P_R xi) P_L xii) P_C xiii) Real power,
 xiv) Reactive power xv) Apparent power xvi) power factor

Sol:- $X_L = 5\Omega$; $X_C = 2\Omega$; $X = X_L - X_C = 3\Omega$ (Inductive)

iv) $|Z| = \sqrt{R^2 + (X_L - X_C)^2} = 5\Omega$ ix) $I = \frac{V}{Z} = \frac{12}{5} = 2.4A$.

v) $|Y| = \left| \frac{1}{Z} \right| = \frac{1}{5} \text{ Siemens.}$

vi) $V_L = I X_L = 2.4(5) = 12V$; vii) $V_C = 4.8V = I X_C$.

viii) $V_R = I R = 2.4(4) = 9.6V$.

x) $P_R = I^2 R = 23.04W$.

xi) $P_L = I^2 X_L = 28.8VAR$

xii) $P_C = I^2 X_C = 11.52VAR$.

xvi) power factor = $\frac{R}{Z} = \frac{4}{5} = 0.8 \text{ (lag)} = \cos\phi$.

$X_L > X_C$ so $I \text{ lag } V$.

$\sin\phi = \sqrt{1 - \cos^2\phi} = \sqrt{1 - 0.8^2} = 0.6$.

xiii) Real power = $P_R = \text{Avg. power} = V_{rms} I_{rms} \cos\phi$.
 $= VI \cos\phi = 23.04W$

xiv) Reactive power = $P_L - P_C = V_{rms} I_{rms} \sin\phi = 17.28VAR$.

xv) Apparent power = $\sqrt{P_R^2 + (P_L - P_C)^2} = V_{rms} I_{rms} = VI = 28.8VA$