

TRANSFORMER

Transformer :-

- A transformer is a static piece of equipment used for either raising or lowering the voltage of an ac supply with a corresponding decrease or increase in current.
- It consists of two windings, primary winding and secondary winding.
- These windings are wound on a common laminated magnetic core.
- The winding connected to A.C. supply is called primary winding and the one connected to load is called secondary winding.
- The alternating voltage V_p whose magnitude to be changed is applied to primary and Alternating E.M.F induced in the secondary is V_s (or) E_s . (Ideally both are equal in magnitude).
- The current in primary is I_p and in secondary is I_s .
- The no. of turns in primary is N_p and in secondary is N_s .

Working of Transformer :-

- When an alternating voltage V is applied to the primary winding, an alternating flux ϕ is set up in the core.
- This Alternating flux links both the windings and induces the E.M.Fs E_p and E_s in them according to Faraday's law of electromagnetic induction.
- The E.M.F E_p is termed as primary E.M.F and E_s is termed as secondary E.M.F

$$E_p = -N_p \cdot \frac{d\phi}{dt}$$

$$E_s = -N_s \cdot \frac{d\phi}{dt}$$

$$\therefore \boxed{\frac{E_s}{E_p} = \frac{N_s}{N_p}} \longrightarrow \textcircled{1}$$

→ The Magnitudes of E_s and E_p depends on number of turns on Secondary and primary.

TYPES of Transformer :-

Step up transformer :-

The transformer in which primary voltage is less than secondary voltage (or) primary turns are less than secondary turns is known as step up transformer.

i.e. $\boxed{N_p < N_s}$ or $\boxed{I_p > I_s}$ or $\boxed{E_p < E_s}$

Step down transformer :-

The transformer in which primary voltage is greater than secondary voltage (or) primary turns are greater than secondary turns is known as step down transformer.

i.e. $\boxed{N_p > N_s}$ or $\boxed{E_p > E_s}$ or $\boxed{I_p < I_s}$

An Isolation transformer :-

An Isolation transformer passes the signal unchanged. (Refer Ear/gates)

i.e. $\boxed{N_p = N_s}$ or $\boxed{E_p = E_s}$ or $\boxed{I_p = I_s}$

THEORY OF AN IDEAL TRANSFORMER :-

In an Ideal transformer, the following cases will occur

- i) No winding Resistance
- ii) No leakage flux
- iii) No iron losses.

In transformer (Ideal), the input power = output power.

i.e $E_p I_p = E_s I_s$.

$$\Rightarrow \boxed{\frac{E_p}{E_s} = \frac{I_s}{I_p}} \rightarrow (2)$$

From Eq (1) and Eq (2).

$$\boxed{\frac{E_s}{E_p} = \frac{N_s}{N_p} = \frac{I_p}{I_s}}$$

Note :- A transformer changes the voltage and current of AC only but it can't change their frequency.

TURN'S RATIO :-

The turns ratio is the number of turns in the secondary winding divided by the number of turns in the primary winding. It can be expressed as following :

$$\boxed{\text{Turn's Ratio} = \frac{N_s}{N_p}}$$

As per Earl gate Text book.

Relation Between Input and output impedances :-

$$Z_i = \frac{E_p}{I_p} ; \quad Z_o = \frac{E_s}{I_s}$$

where

Z_o = load Impedance

Z_i = Source

Impedance.

$$\frac{Z_o}{Z_i} = \frac{E_s}{E_p} \cdot \frac{I_p}{I_s}$$

$$= \frac{E_s}{E_p} \cdot \frac{I_p}{I_s} = \frac{N_s}{N_p} \cdot \frac{N_s}{N_p} = \left(\frac{N_s}{N_p}\right)^2$$

$$\boxed{\frac{Z_o}{Z_i} = \left(\frac{N_s}{N_p}\right)^2}$$

Applications of Transformer:-

Transformer applications include:

- i) Impedance Matching.
- ii) Phase shifting.
- iii) Isolation.
- iv) Blocking DC while passing AC, and producing several signals at different voltage levels etc..

NUMERICALS :-

Q. A transformer has 500 turns in primary and 1000 turns in Secondary.

If 120 volt ac is applied to primary

(a) What is the Induced Secondary voltage?

(b) Is it step up or step down?

Sol:- (a) $\frac{N_s}{N_p} = \frac{E_s}{E_p} \Rightarrow \frac{1000}{500} = \frac{E_s}{120} \Rightarrow E_s = \frac{1000}{500} \times 120 = 240V_{ac}$

$$E_s = 240 \text{ volt ac}$$

(b) $E_s > E_p$. So It is step up transformer.

Q. A transformer has 500 turns in primary and 1000 turns in Secondary. If the primary has a current of 100 milli amperes, How much current flows in the Secondary?

Sol:- $\frac{N_s}{N_p} = \frac{I_p}{I_s} \Rightarrow \frac{1000}{500} = \frac{100 \times 10^{-3}}{I_s}$

$$\Rightarrow I_s = \frac{500}{1000} \times 100 \times 10^{-3} A = 50 \times 10^{-3} A$$

= 50 milli Ampere.

Q) What must the turns ratio of a transformer be to match a 4-ohm speaker to a 100 Ω source?

Sol:-

$$Z_o = 4\Omega \quad ; \quad Z_i = 100\Omega \quad \frac{N_s}{N_p} = ?$$

$$\frac{Z_o}{Z_i} = \left(\frac{N_s}{N_p} \right)^2 \Rightarrow \frac{N_s}{N_p} = \left(\frac{4}{100} \right)^{1/2} = \left(\frac{1}{25} \right)^{1/2} = \frac{1}{5}$$

NOTE:-

- Transformers are rated in VA. i.e. Volt-Ampere. (8) kVA.
(VIMP MCQ)
i.e. kilo Volt-Ampere.
- If we apply DC voltage to a transformer, output voltage is Zero
(VIMP MCQ)
(8) Transformer coil burns.

IMP QUESTIONS (ETE)

- Explain construction, working, types, Applications of transformer and its numericals.
Refer: Text book for diagrams and theory.

In ETE exam, write diagrammatic explanation and more diagrams of transformer.

