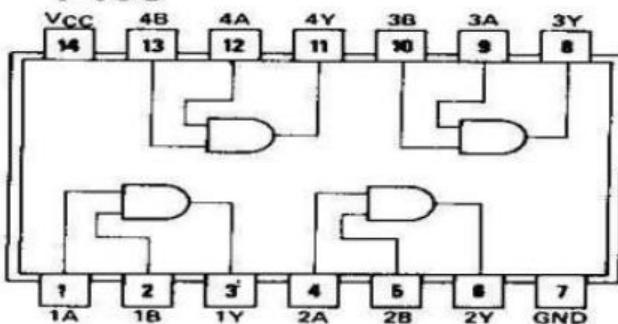


DIGITAL ELECTRONICS
LABORATORY
ECE-279


EXPERIMENT :- 6

To analyse and implement Boolean expression using basic logic
(AND, OR, NOT, NAND, NOR, XOR, XNOR)


7408




7432

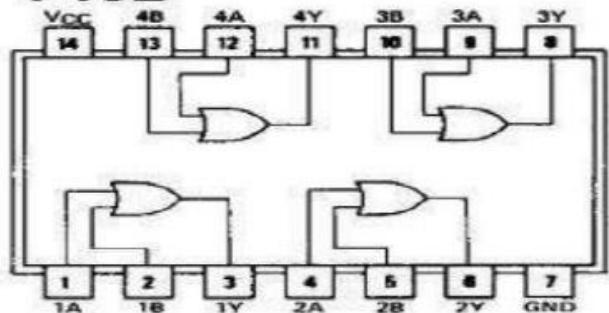


7486

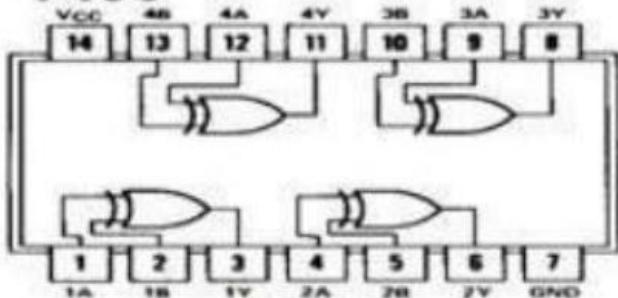


7404

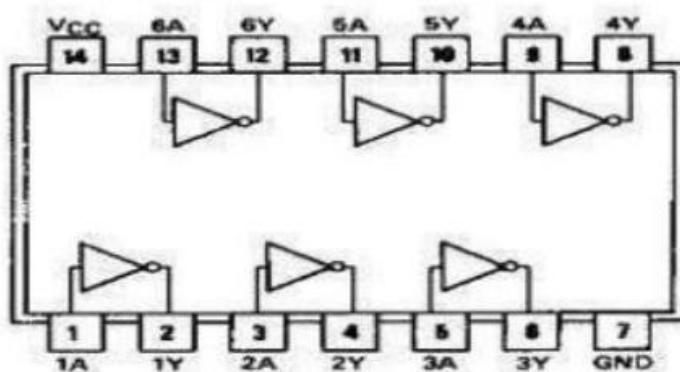

7402

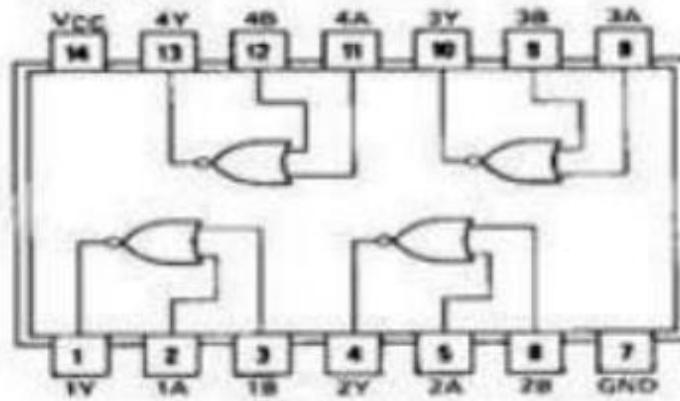


7400

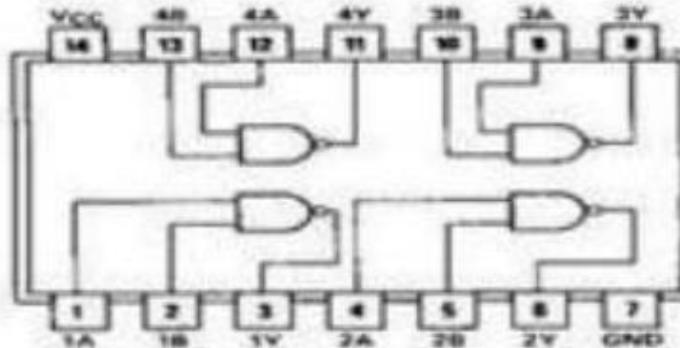


Implement boolean equation

$$AB + A'C + BC = AB + A'C$$

L.H.S

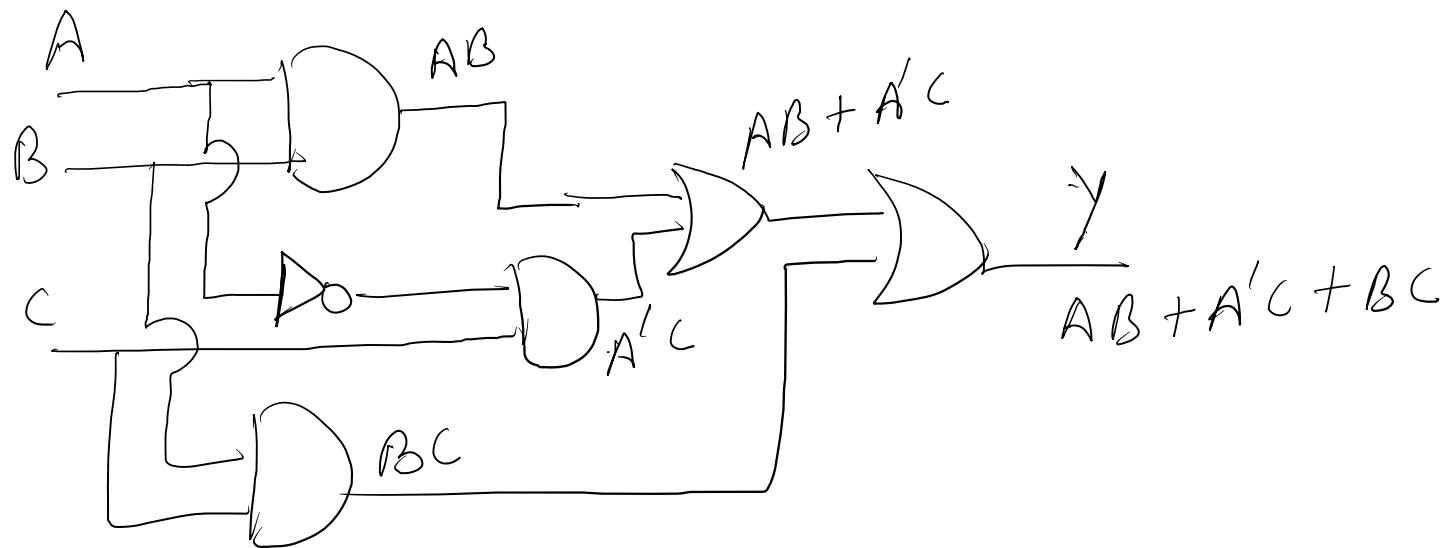


R.H.S

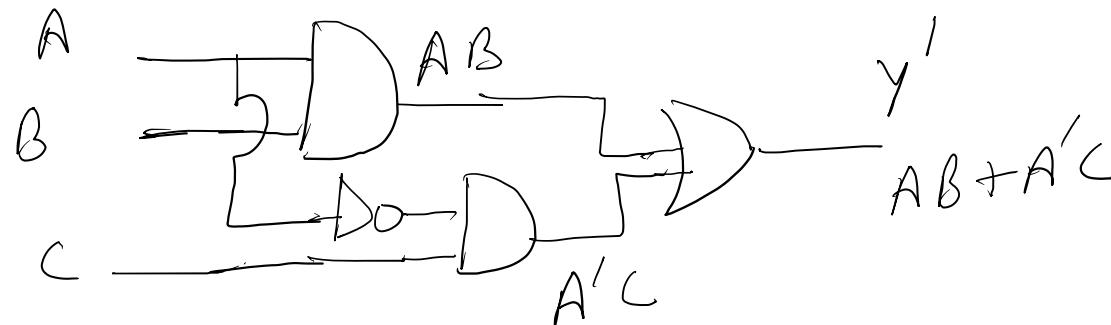

Truth Table

A	B	C	A'	AB	A'C	BC	Y'=AB+A'C +BC	Y=AB+A'C +BC
0	0	0	1	0	0	0	0	0
0	0	1	1	0	1	0	1	1
0	1	0	1	0	0	0	0	0
0	1	1	1	0	1	1	1	1
1	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	1	0	0	1	0	0	1	1
1	1	1	0	1	0	1	1	1

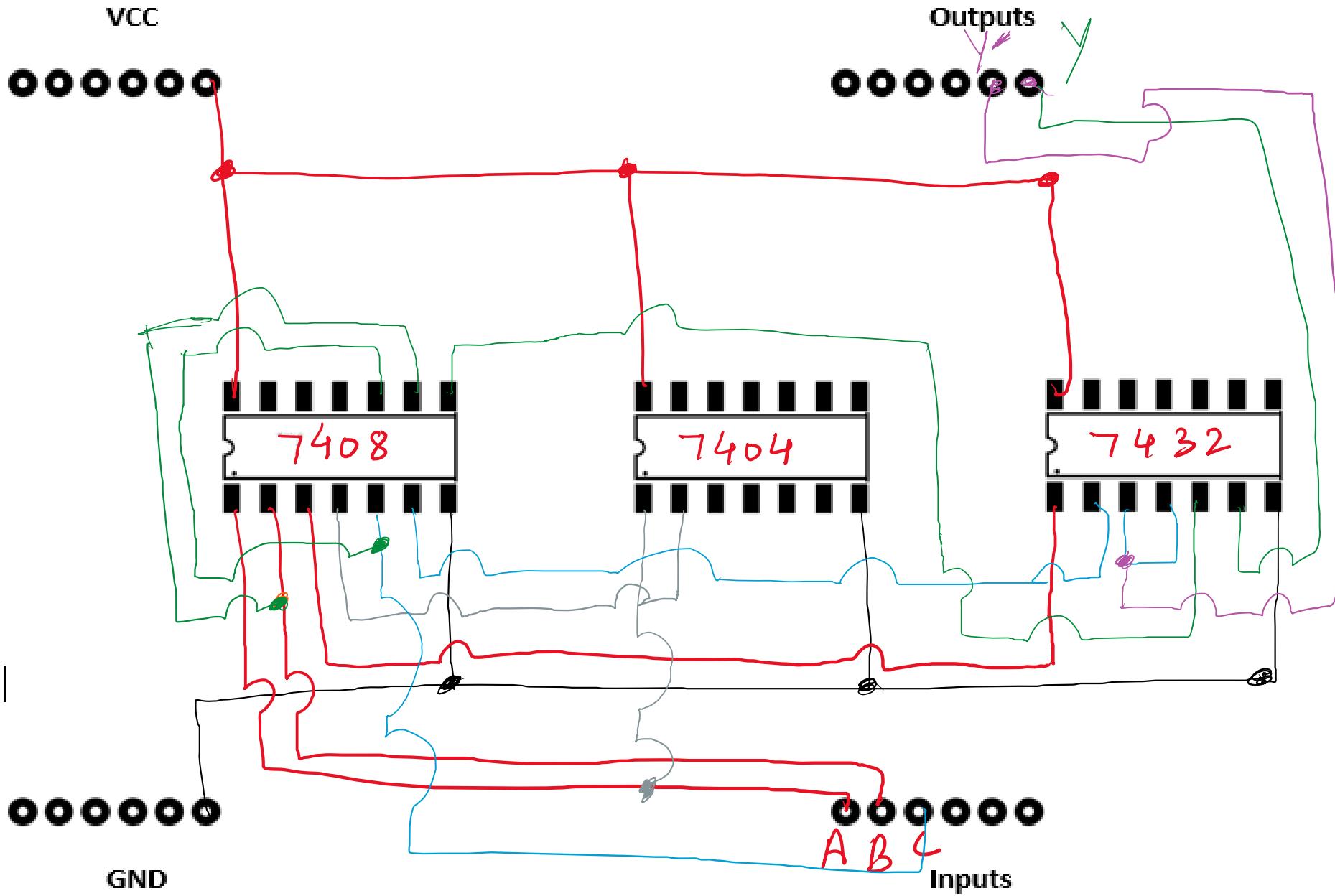Implement boolean equation
 $AB + A'C + BC = AB + A'C$





EXPERIMENT :- 7


To design a circuit for full Adder and full Subtractor using XOR and basic gates

1). Full Adder using two half adders

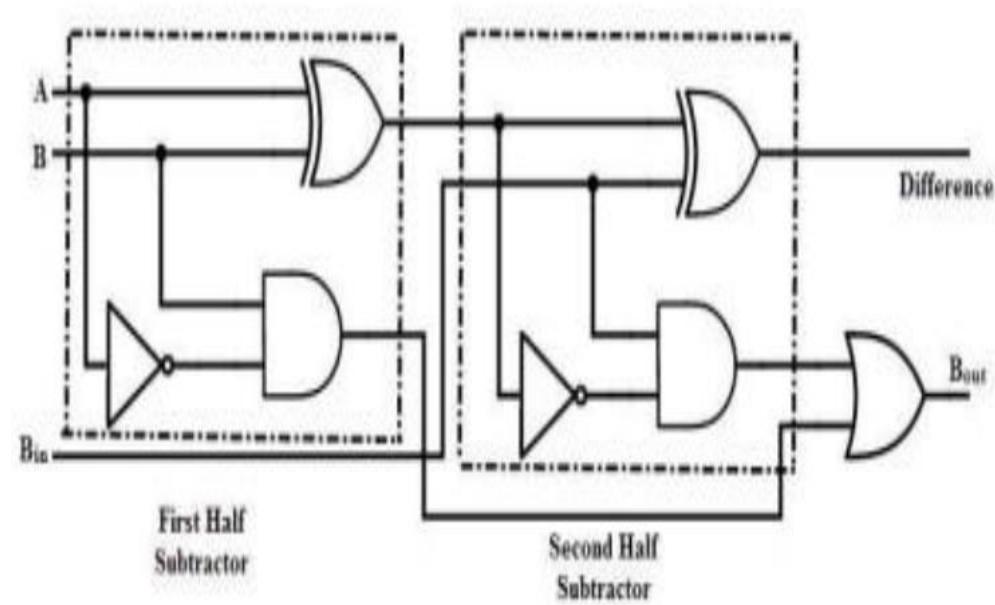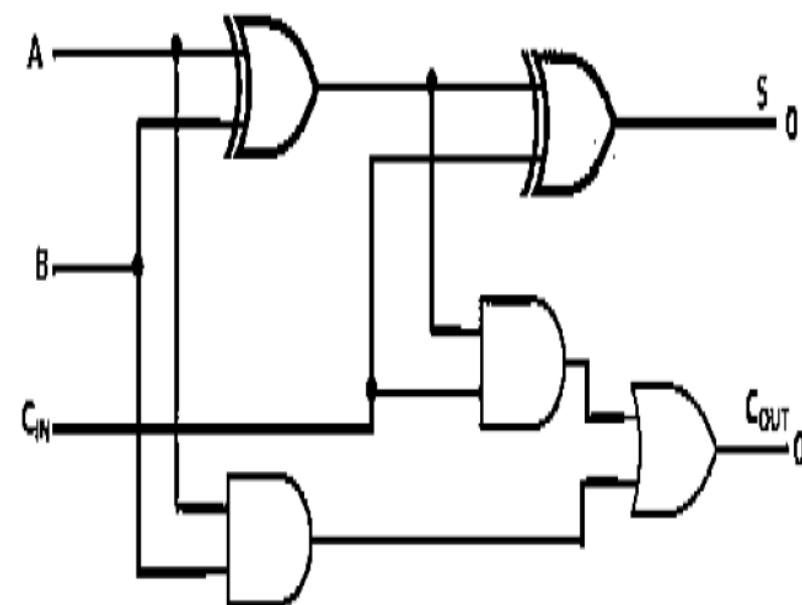2). Full Subtractor using two half subtractor




HALF ADDER →

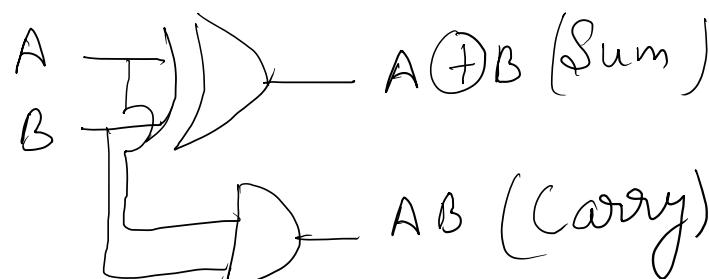

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half Subtractor →

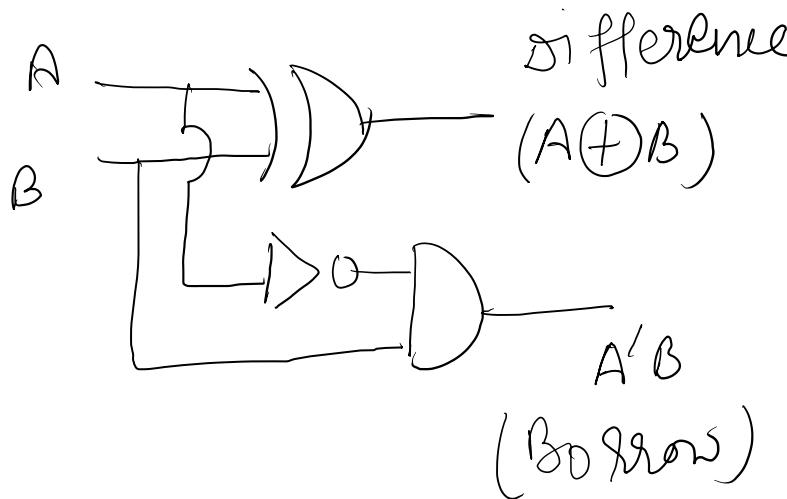

A	B	Diffl.	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Full Adder

Sum $\rightarrow \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} \bar{C} + A B C$

$$= C(\bar{A} \bar{B} + A B) + \bar{C} (\bar{A} B + A \bar{B})$$
$$= C(\overline{A \oplus B}) + \bar{C} (A \oplus B)$$
$$= A \oplus B \oplus C$$

Carry $\rightarrow \bar{A} B C + A \bar{B} C + A B \bar{C} + A B C$

$$= C(\bar{A} B + A \bar{B}) + A B (\bar{C} + C) \quad (\because \bar{C} + C = 1)$$
$$= C(A \oplus B) + A B$$

Full Subtractor

Difference $\Rightarrow \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} \bar{C} + A B C$

$$\Rightarrow C(\bar{A} \bar{B} + AB) + \bar{C}(\bar{A} B + A \bar{B})$$
$$\Rightarrow C(\overline{A \oplus B}) + \bar{C}(A \oplus B)$$
$$\Rightarrow A \oplus B \oplus C$$

Borrow $\rightarrow \bar{A} \bar{B} C + \bar{A} B \bar{C} + \bar{A} B C + A B C$

$$\Rightarrow C(\bar{A} \bar{B} + AB) + \bar{A} B (\bar{C} + C) \quad (\because \bar{C} + C = 1)$$
$$\Rightarrow C(\overline{A + B}) + \bar{A} B (1)$$
$$= C(\overline{A + B}) + \bar{A} B$$


Full Adder truth table


A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Subtractor truth table

A	B	C	Diff.	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


FULL ADDER

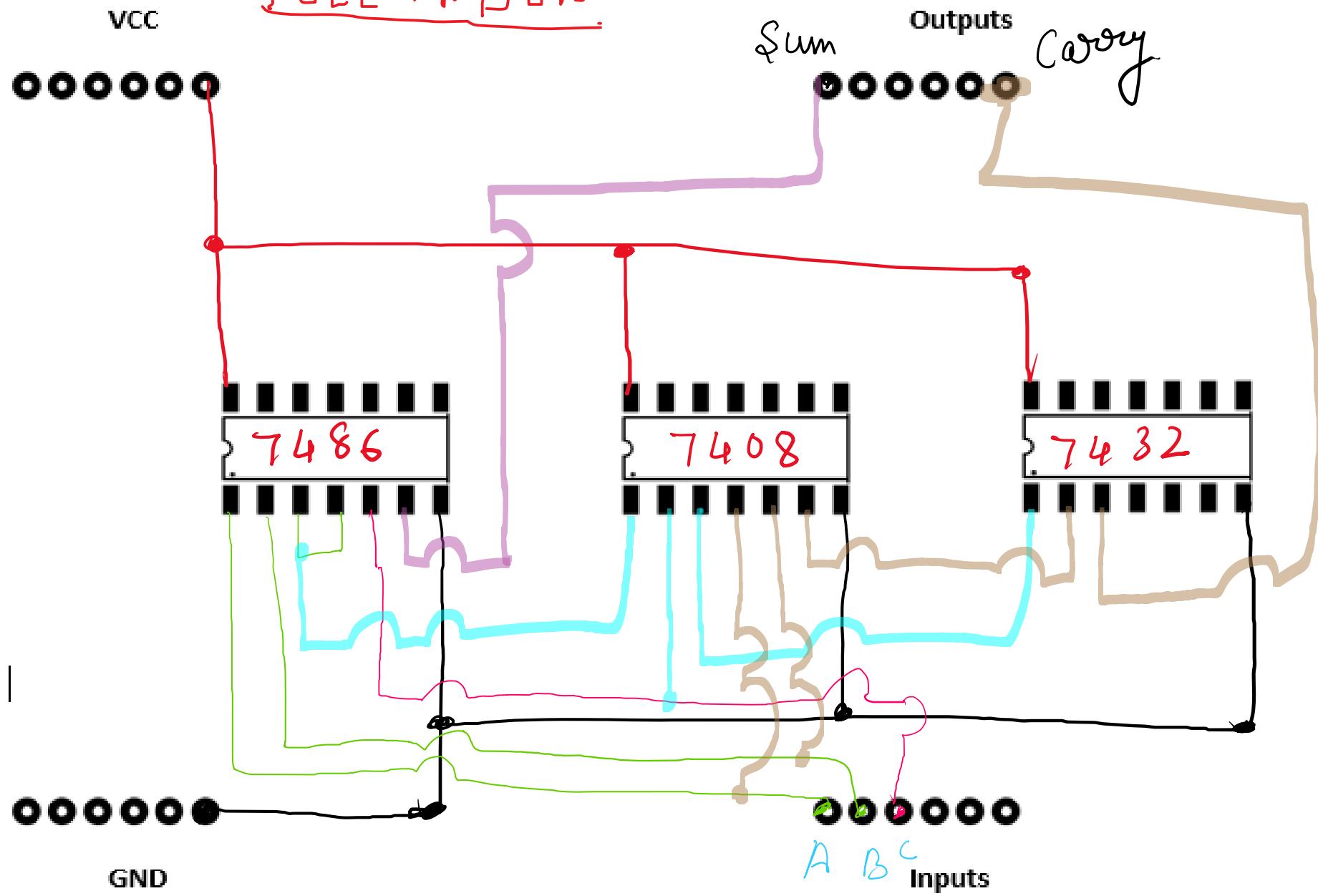

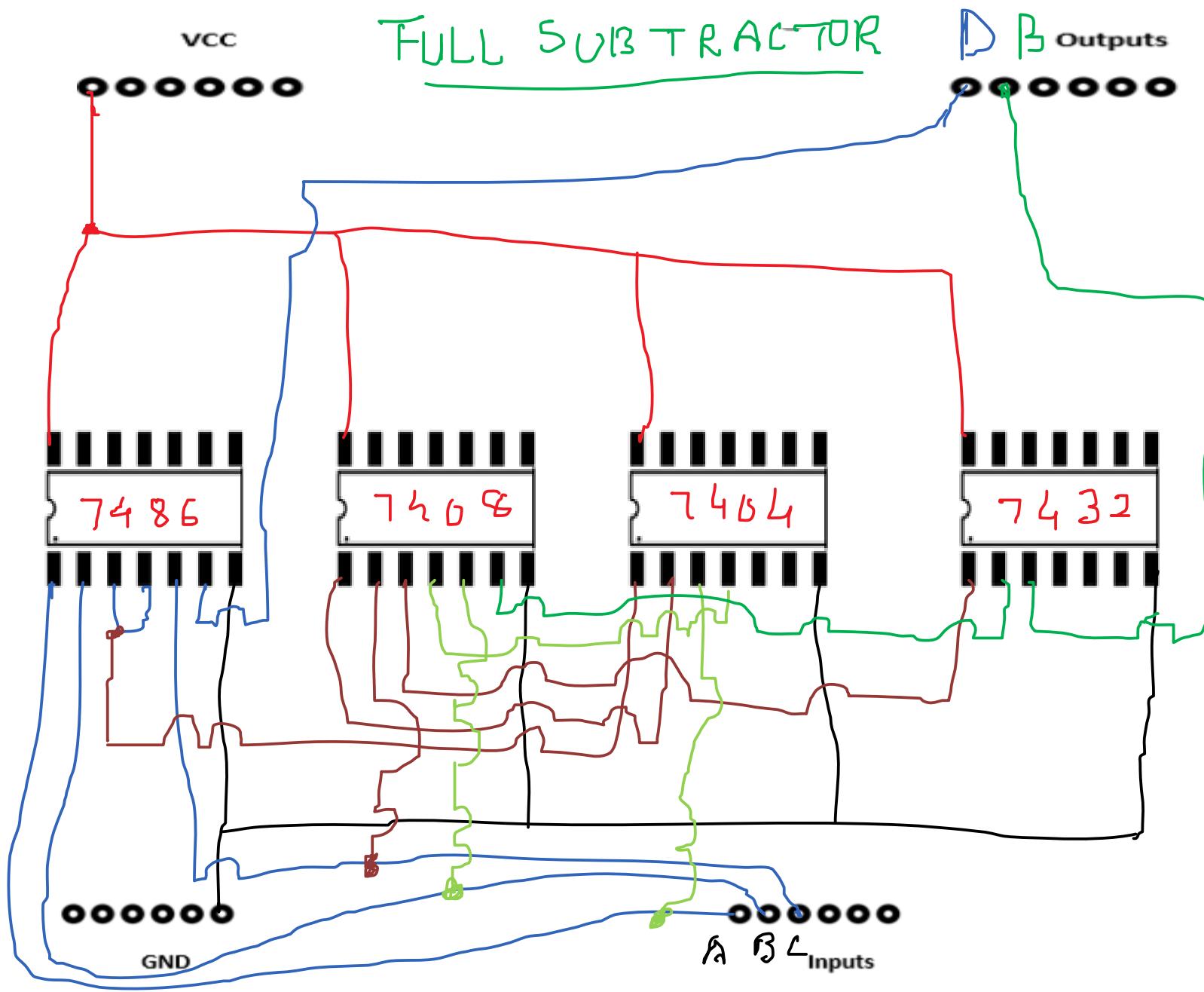


EXPERIMENT :- 8

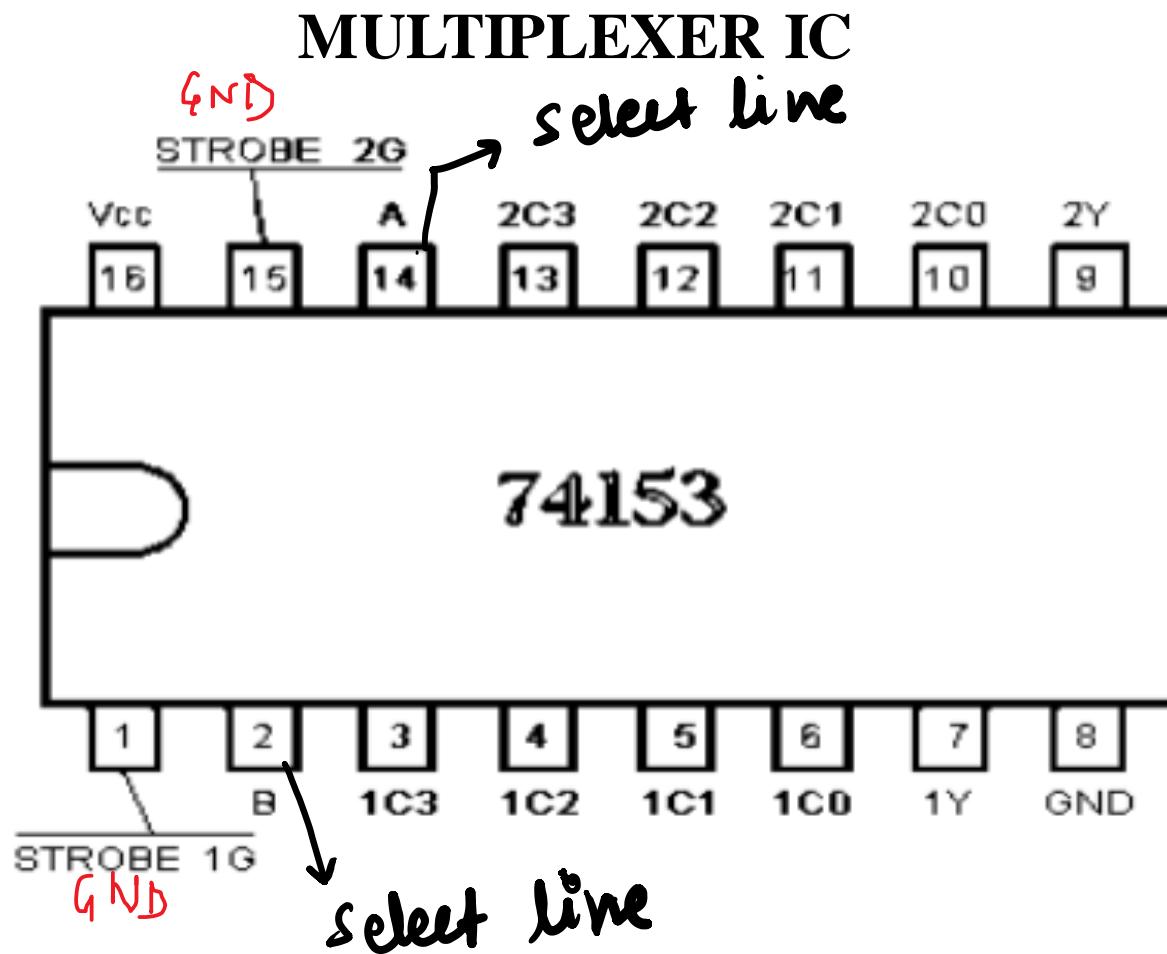1. Aim: To design a circuit to implement Boolean functions using Multiplexers.
2. Aim: To design a circuit to implement Boolean functions using Decoders.





3:8 DECODER IC

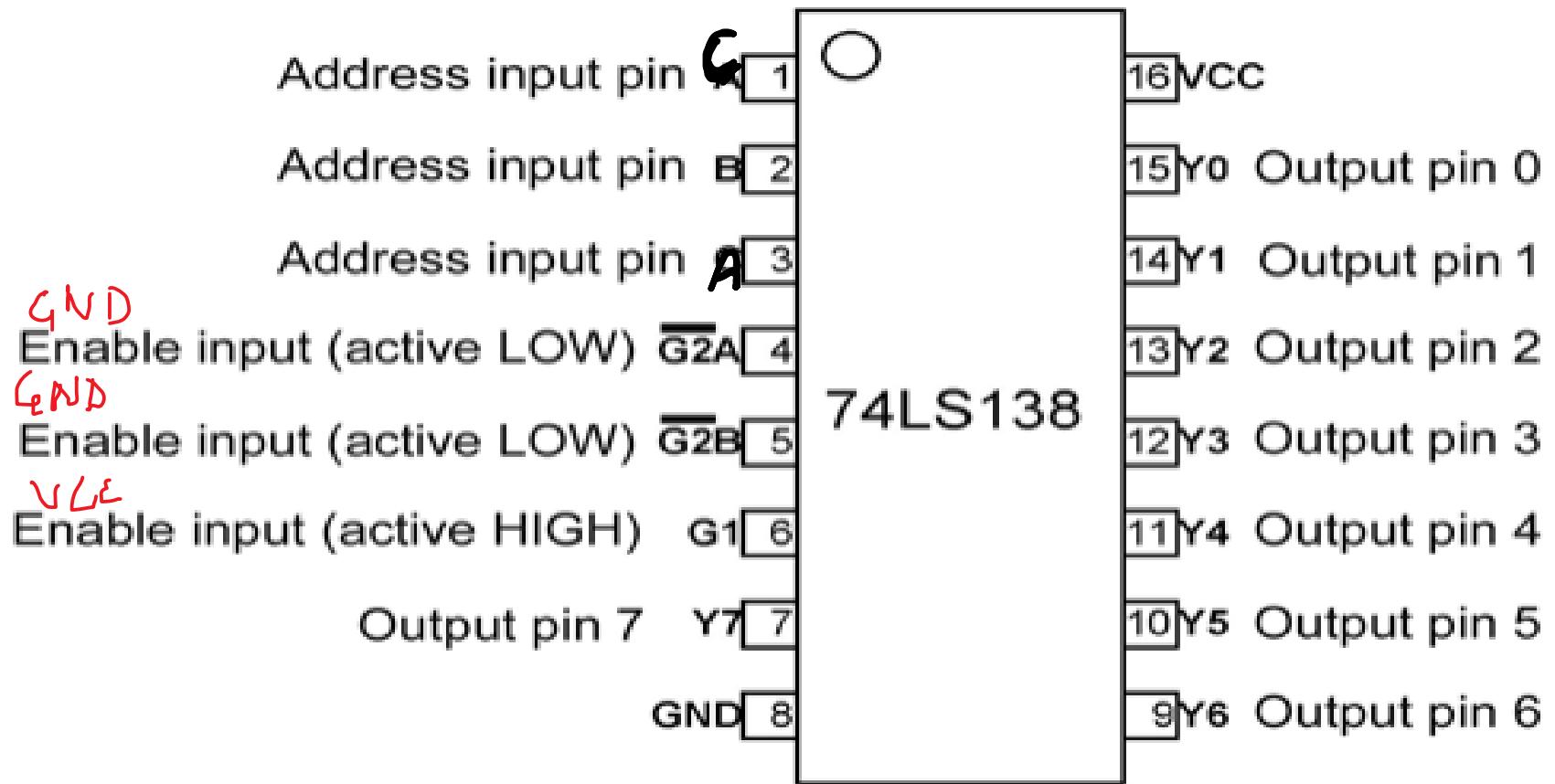


Multiplexer $\rightarrow \Sigma_m(0, 1, 4, 6)$ (select line BC)

mUX mapping \rightarrow

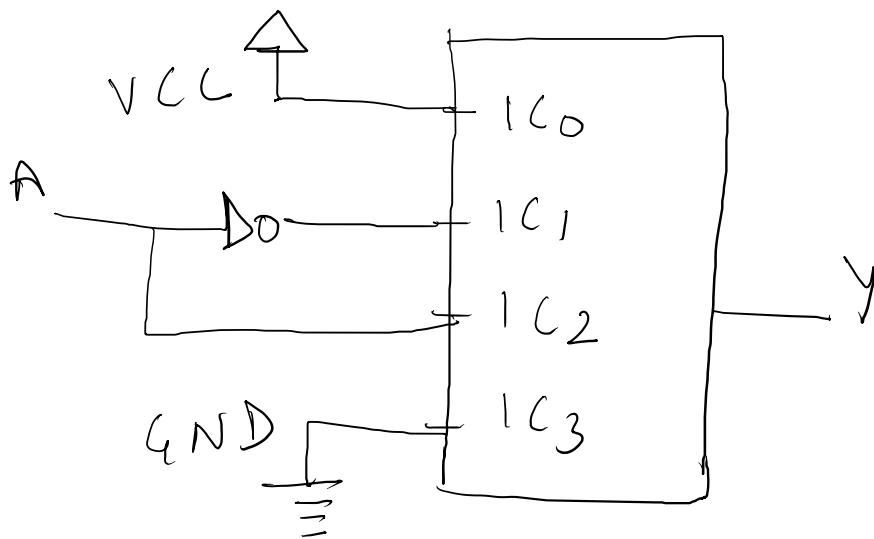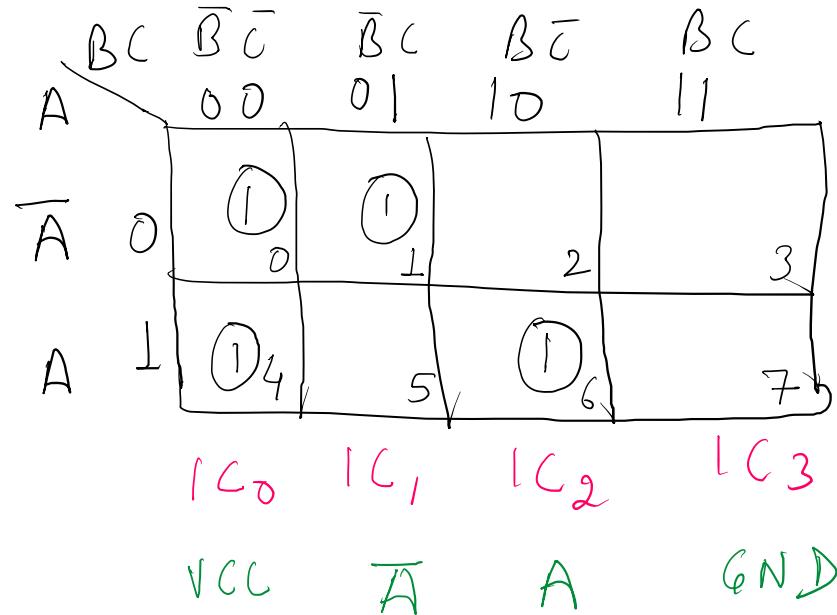

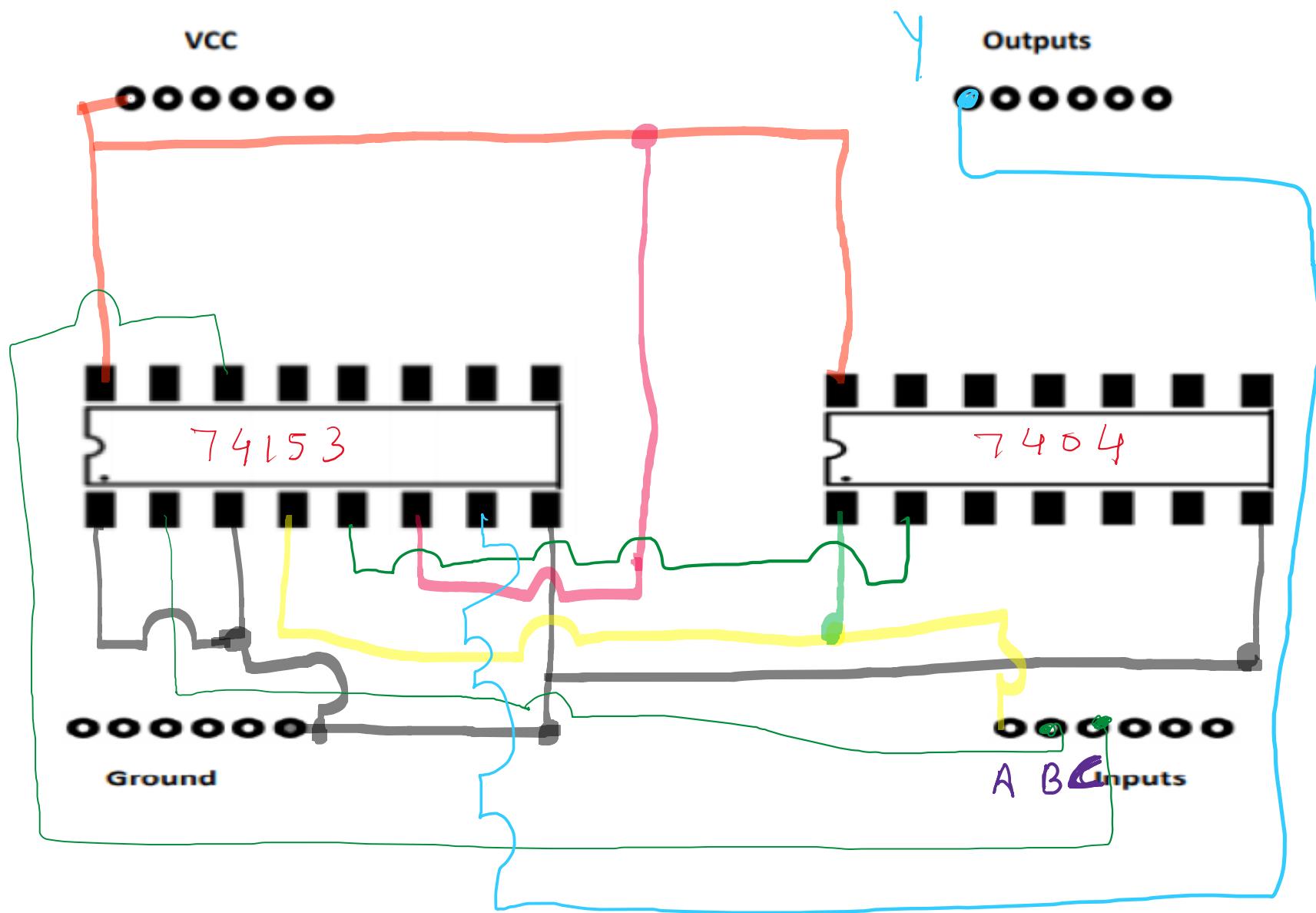
4:1 MUX $\rightarrow \Sigma_m(0, 1, 4, 6)$ select line BC



$\Sigma_m(0, 1, 4, 6)$ (4:1-MUX)

ABC	O/P
000	1
001	1
010	0
011	0
100	1
101	0
110	1
111	0

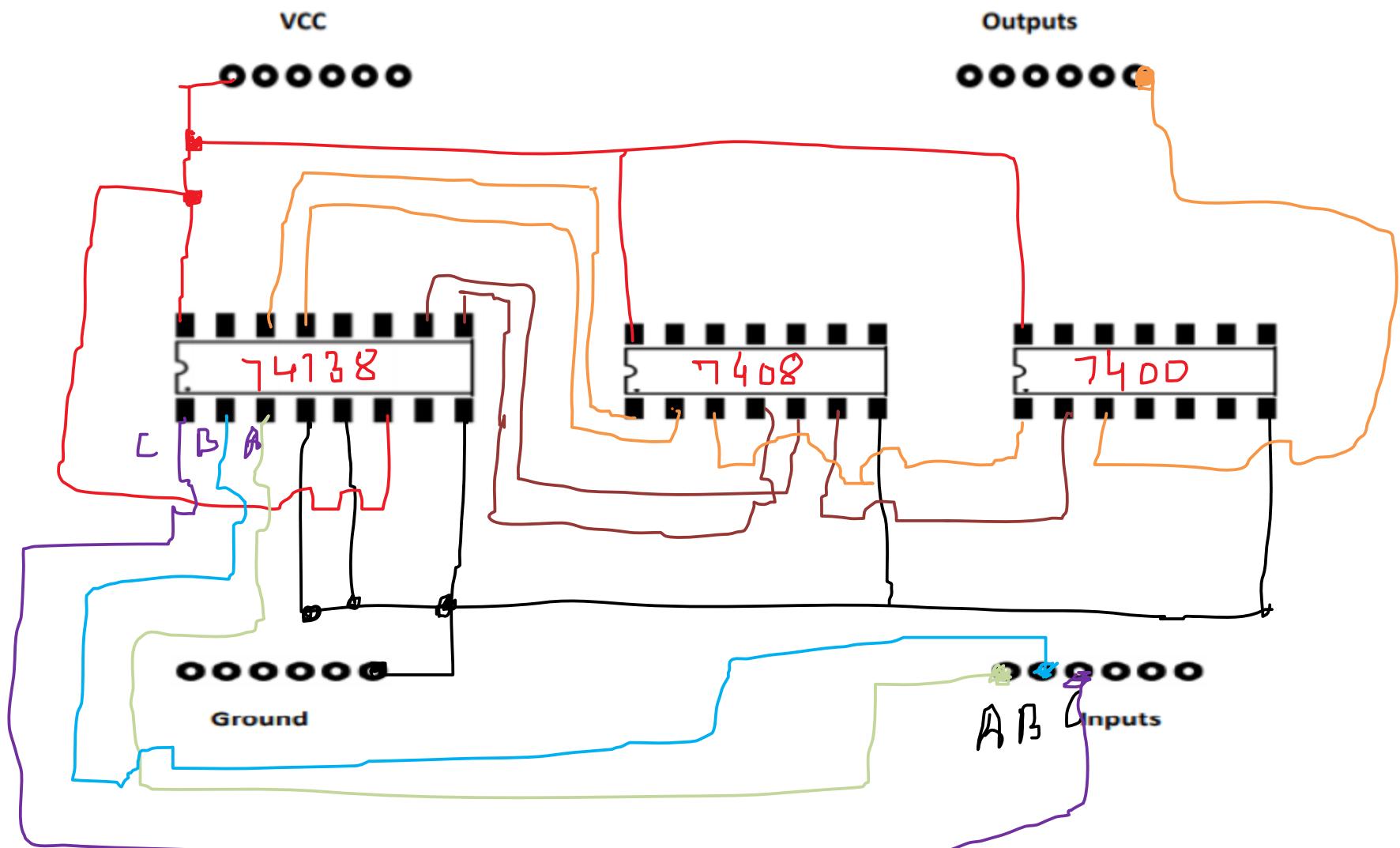3:8 Decoder \rightarrow $\text{Im}\{1, 2, 5, 6\}$




$\Sigma_m [1, 2, 5, 6], \underline{3:8 Decoder}$

Experiment-9

Understanding the sequential logic by implementing the flip flop with the help of logic gates


J-K flip-flop

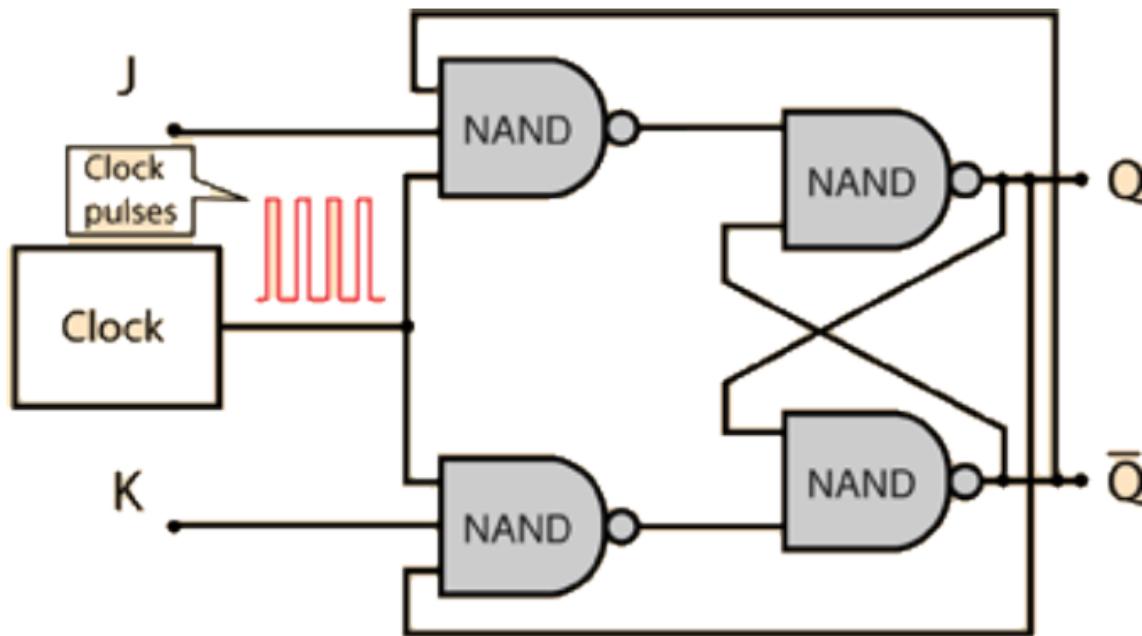


J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

Pin Diagram


7410

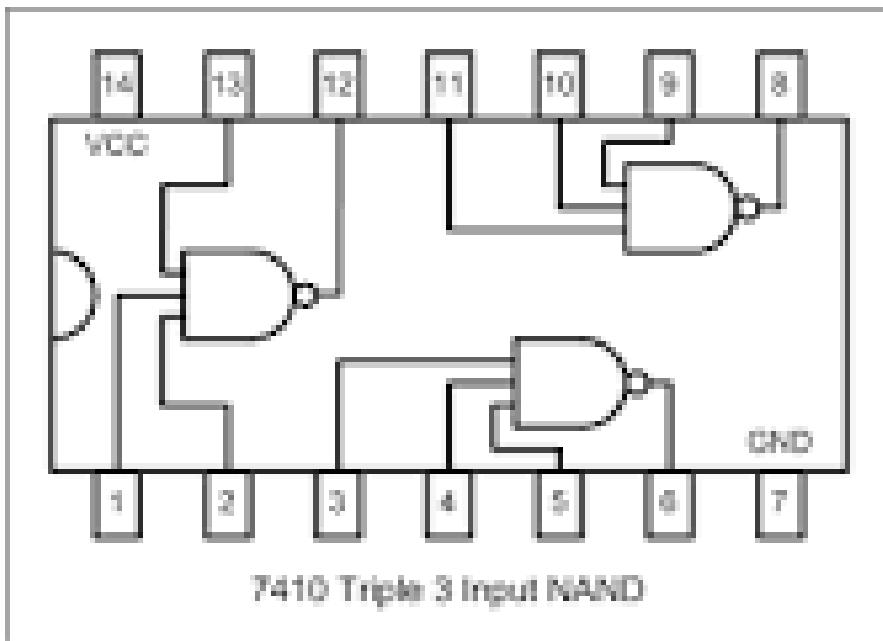

7400

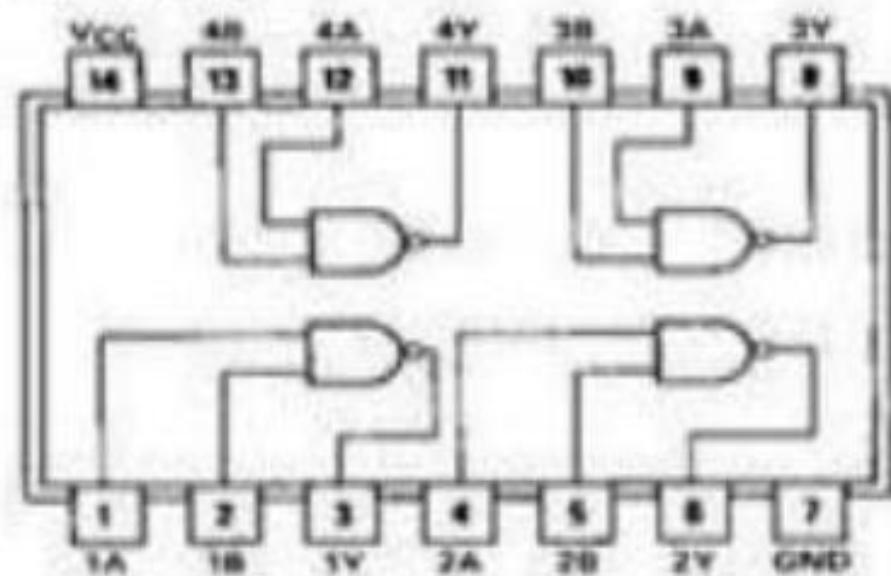


Virtual bread board diagram

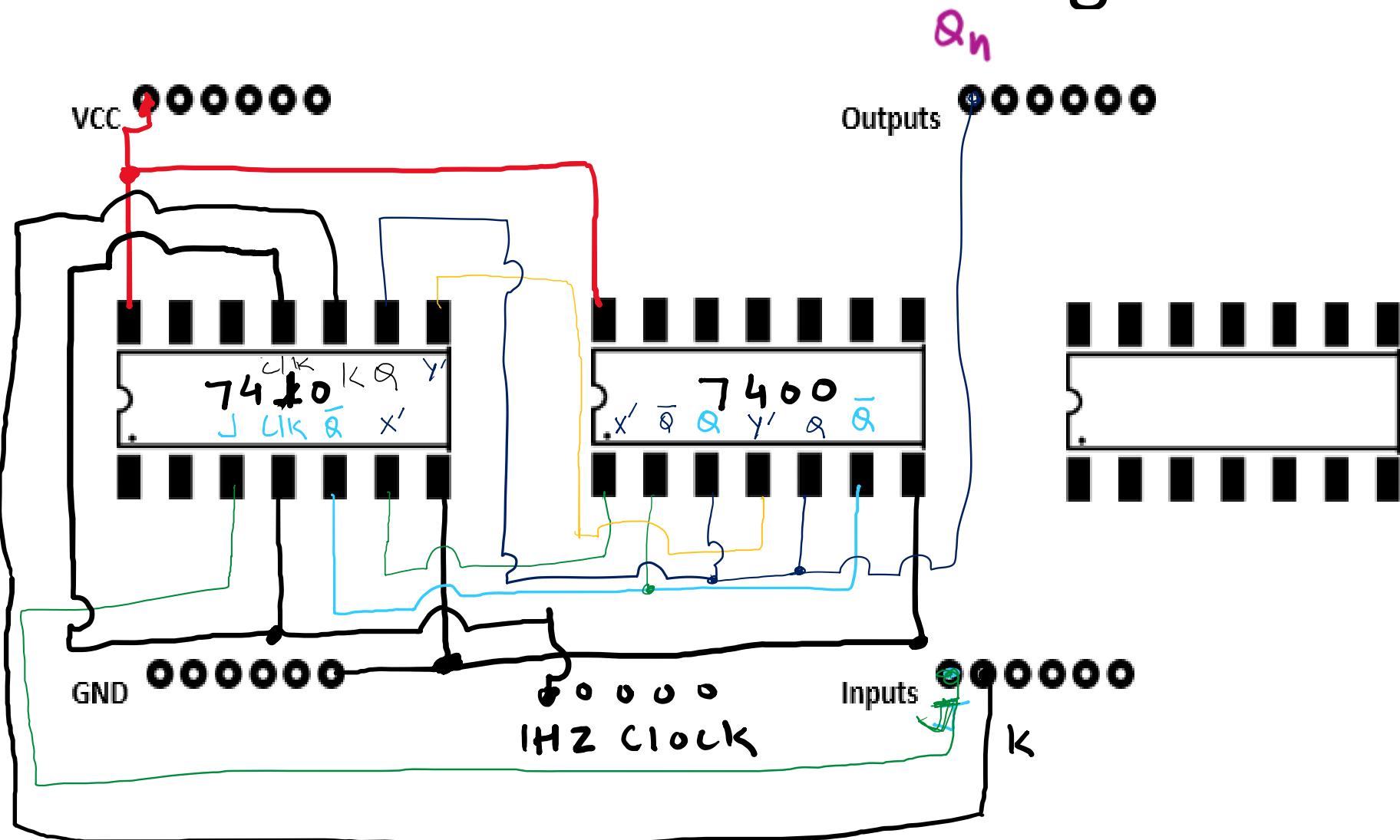

Experiment 10

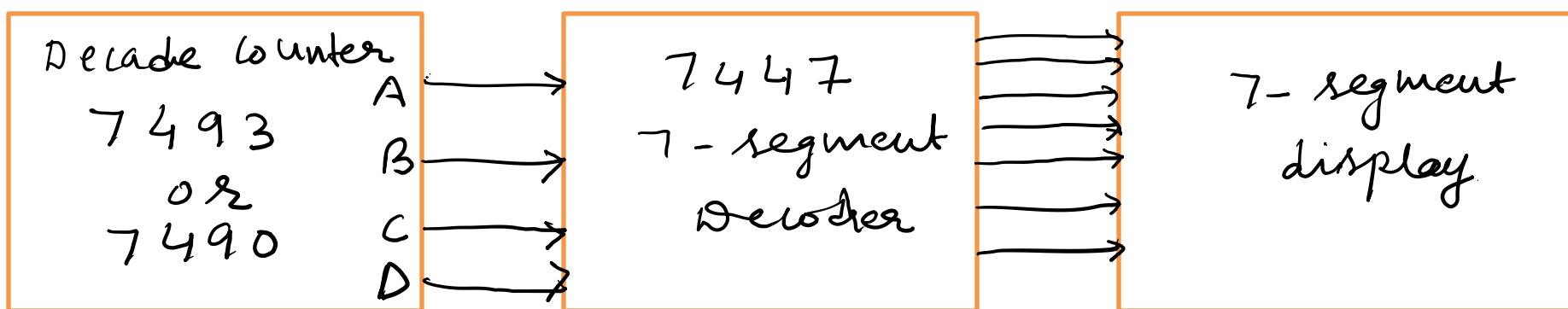
To visualize the output of decade counter on seven segment display




Pin Configuration


NC: Not Connected

7490

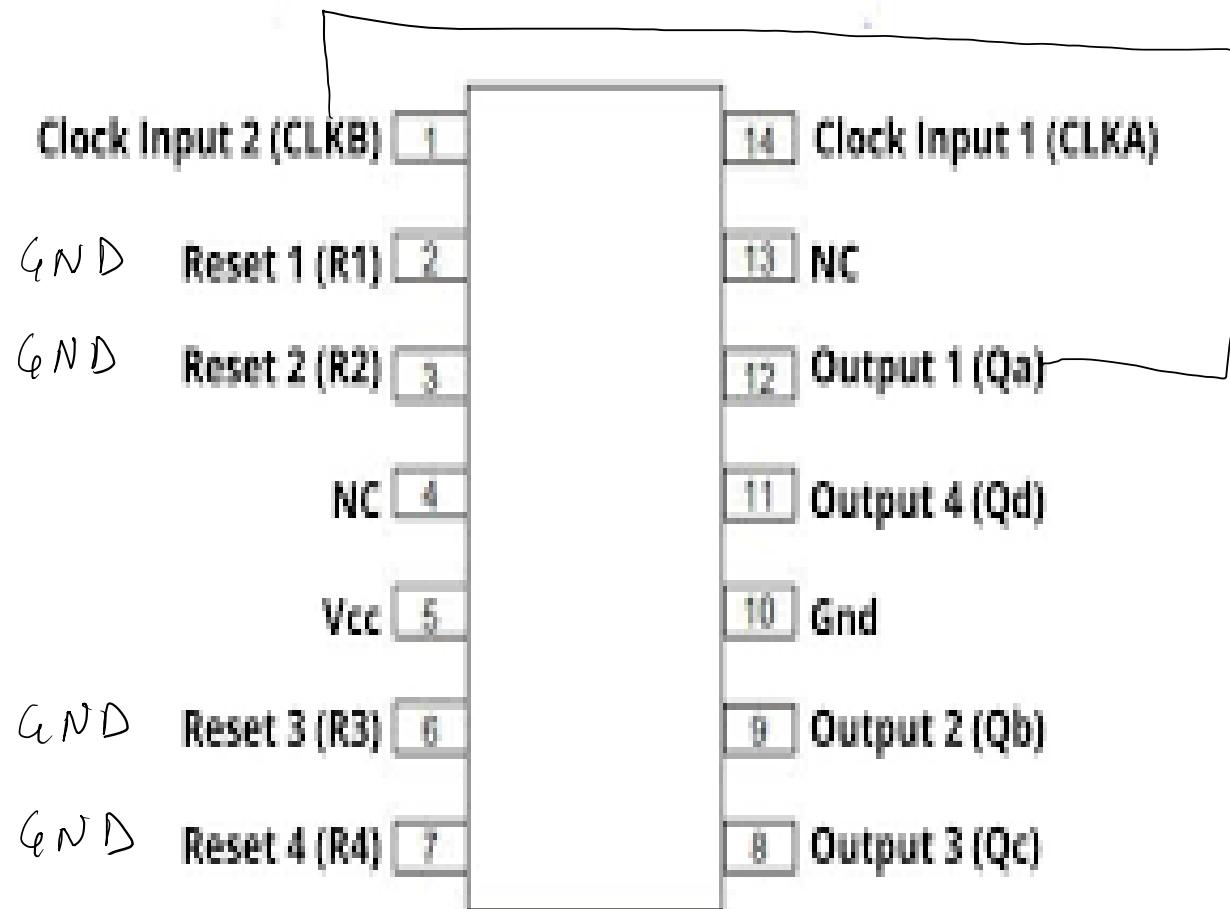


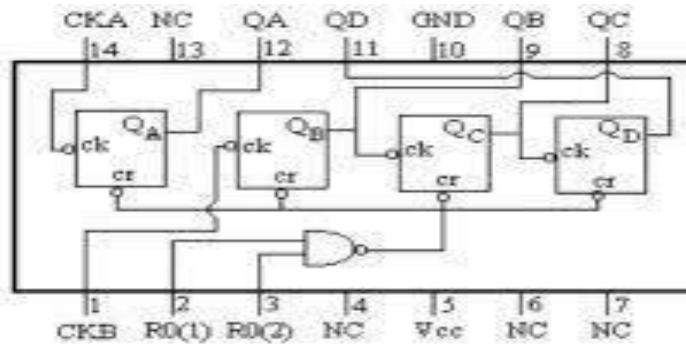


Pin Configuration Connection Diagram

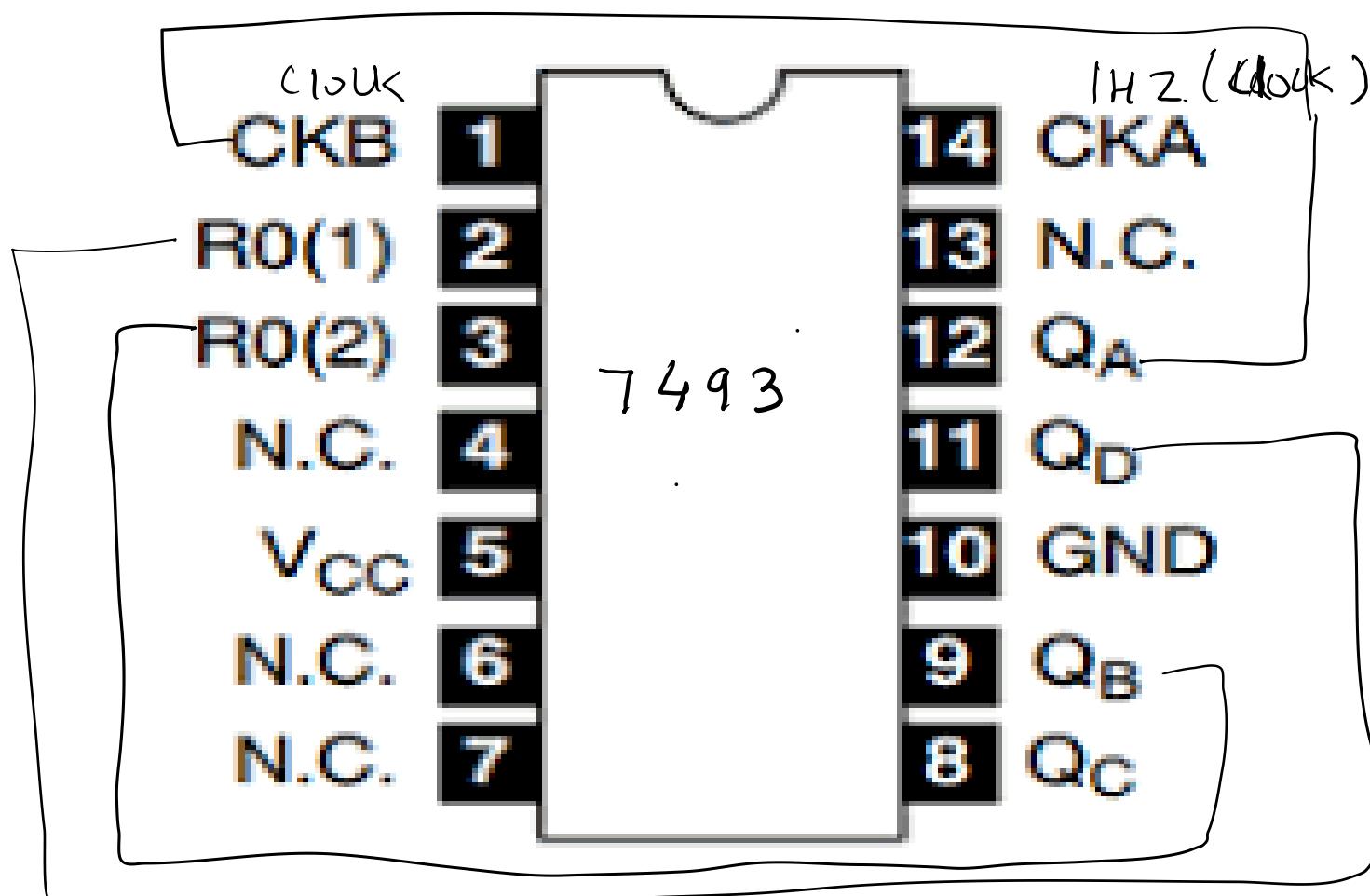

Testing of 7 segment display

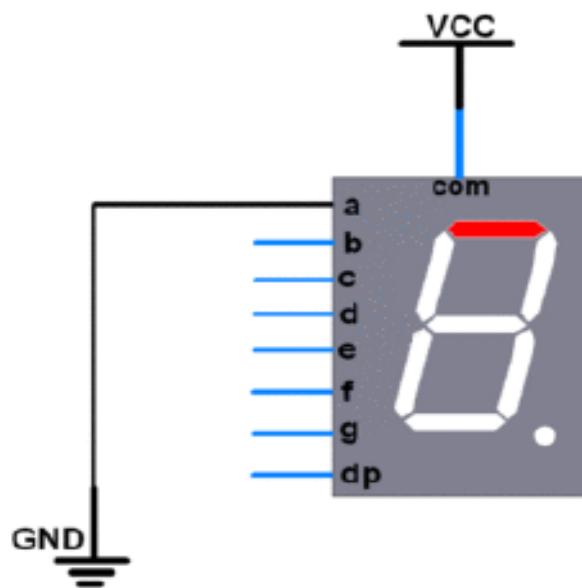

Common Anode

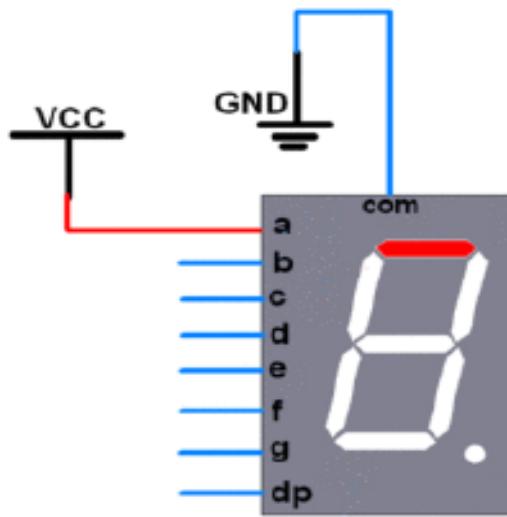

Common Cathode

